
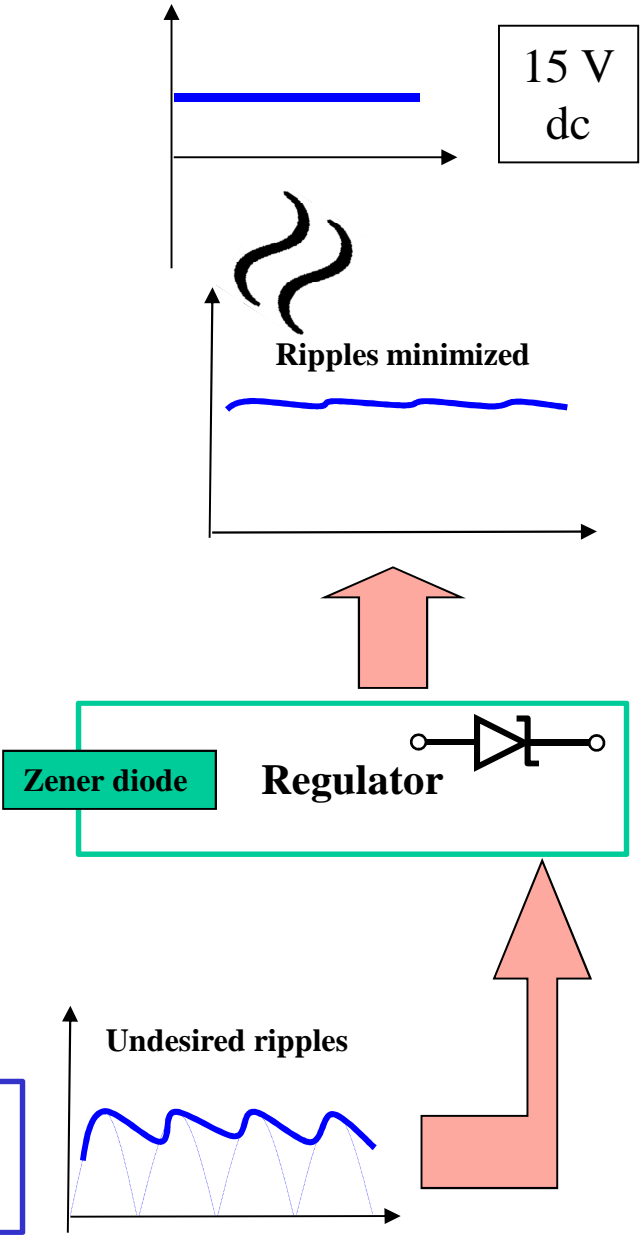


## Rectifier Circuits

Rectifiers are devices that convert AC voltage to DC voltage. They use the diodes and make advantage of their characteristic that allows current to flow only in one direction.


# Basic Components

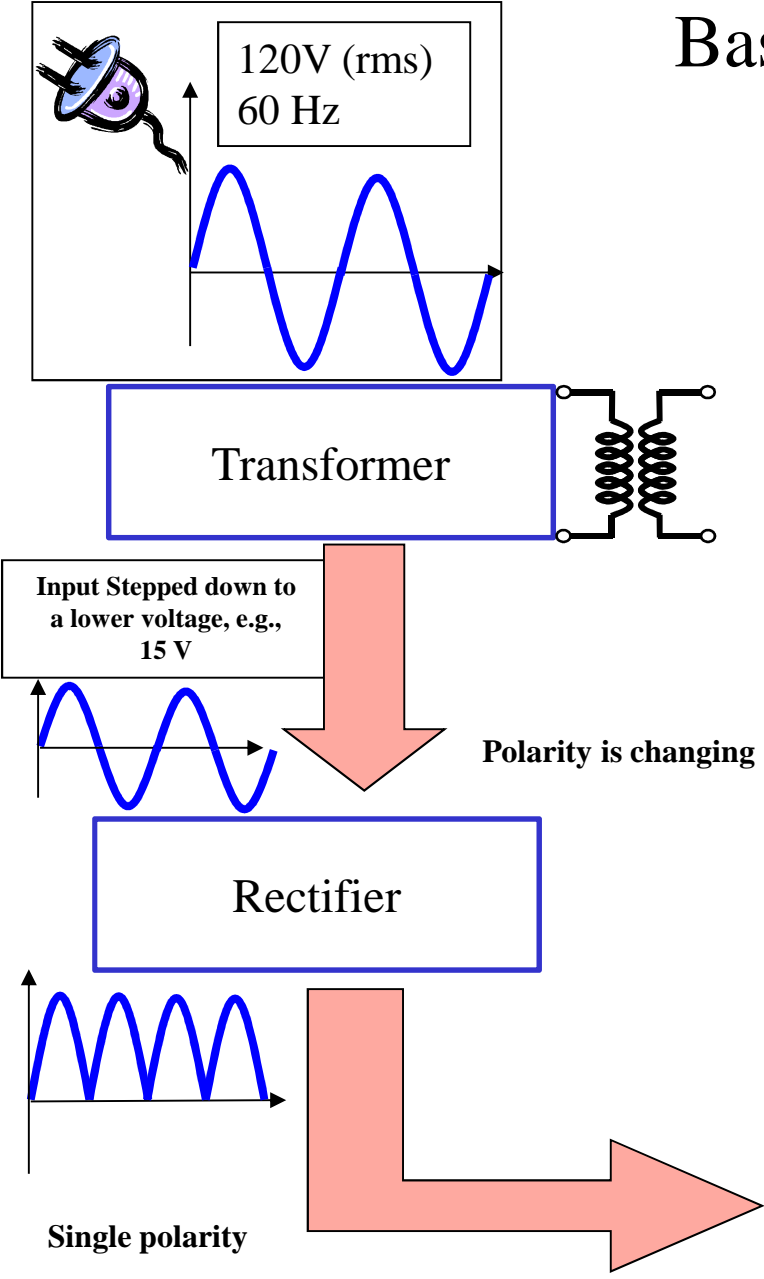


# Half-Wave Rectifier

$$v_o = v_s - V_D$$


$$PIV = V_s$$

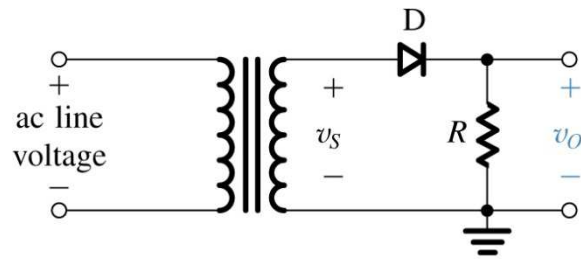


(a)

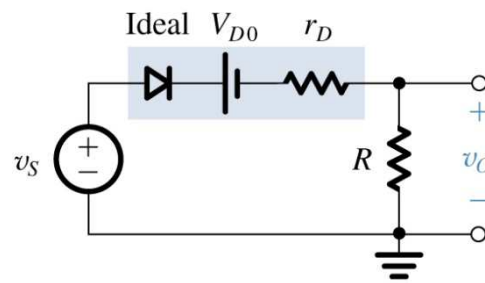

(b)

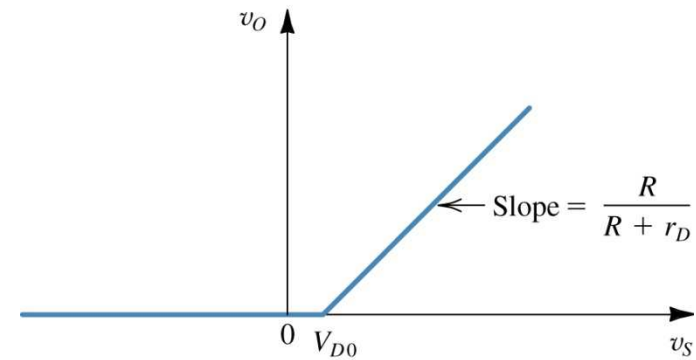

(c)

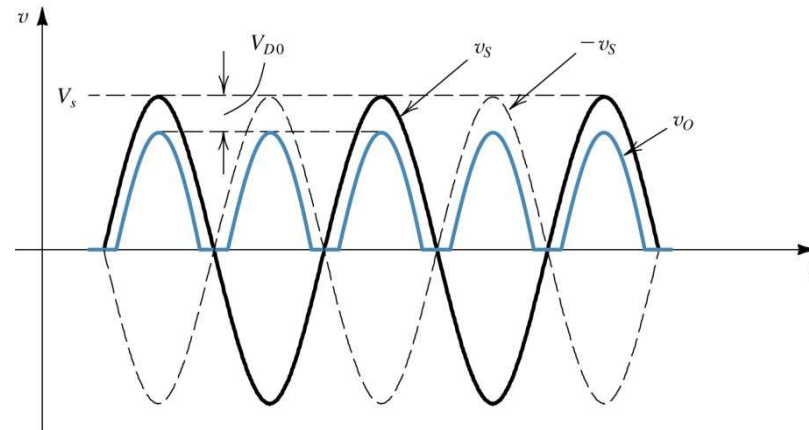


(c)

# Breakdown

## How or when can it occur?

Diodes are usually marked by their **PIV** rating. A diode with low PIV rating (i.e., one that breaks down at small negative voltage) is cheaper and easier to manufacture, while another one that has a high PIV rating can sustain a large negative voltage without breakdown

## What is PIV?

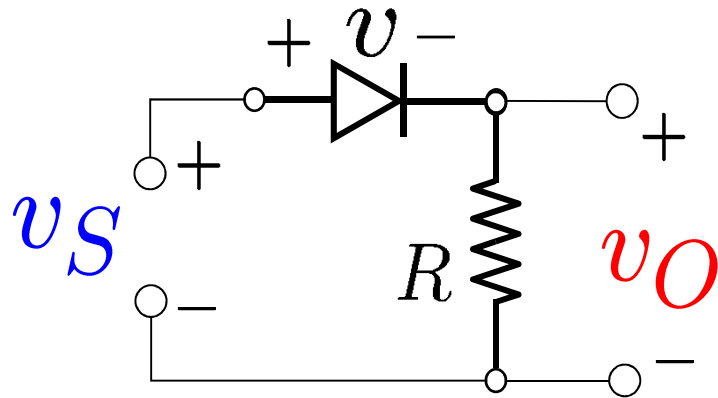

The **PIV** for this half-wave single diode rectifier is the peak value


$$\text{PIV} = |v_{\min}| = | -V_S | = V_S$$

In other words, to design a half-wave rectifier using a single diode, we need to use a diode whose **PIV** is higher than  $V_S$ , which is the peak value of the source voltage


For example, if  $V_S$  is 10 V, then it would be safer to choose a diode whose  $V_{ZK}$  higher than, e.g. is 40 % bigger than  $V_S$

# Full-Wave Rectifier


$$PIV = 2V_s - V_{D0}$$

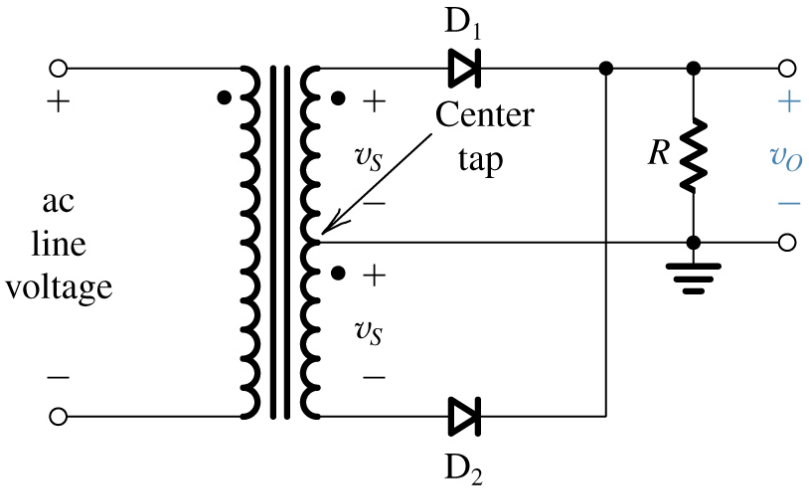

(a)

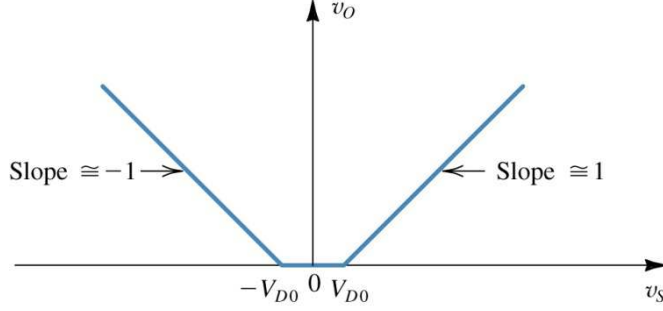

(b)

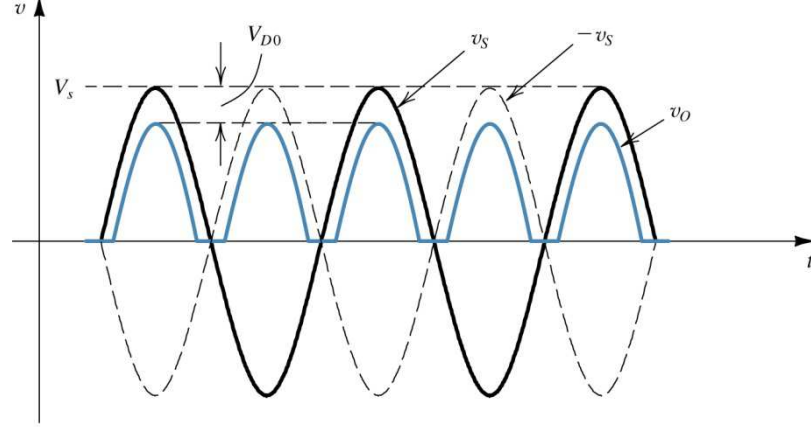

(c)

# Comparison Between Half- and Full Wave Rectifier in terms of the PIV

$$\text{PIV}_{(\text{One-diode Half-Wave})} = V_S$$

$$\text{PIV}_{(\text{Two-diode Full-Wave})} = 2V_S - V_{DO}$$

That is bad, because it means  
that we will need to use a diode  
with a higher PIV rating


# Bridge Rectifier

The bridge rectifier acts as a full-wave rectifier. In addition, it does not suffer from the high PIV requirement needed in the two-diode full-wave rectifier presented earlier.




# The Bridge Rectifier

$$PIV = V_s - V_{D0}$$

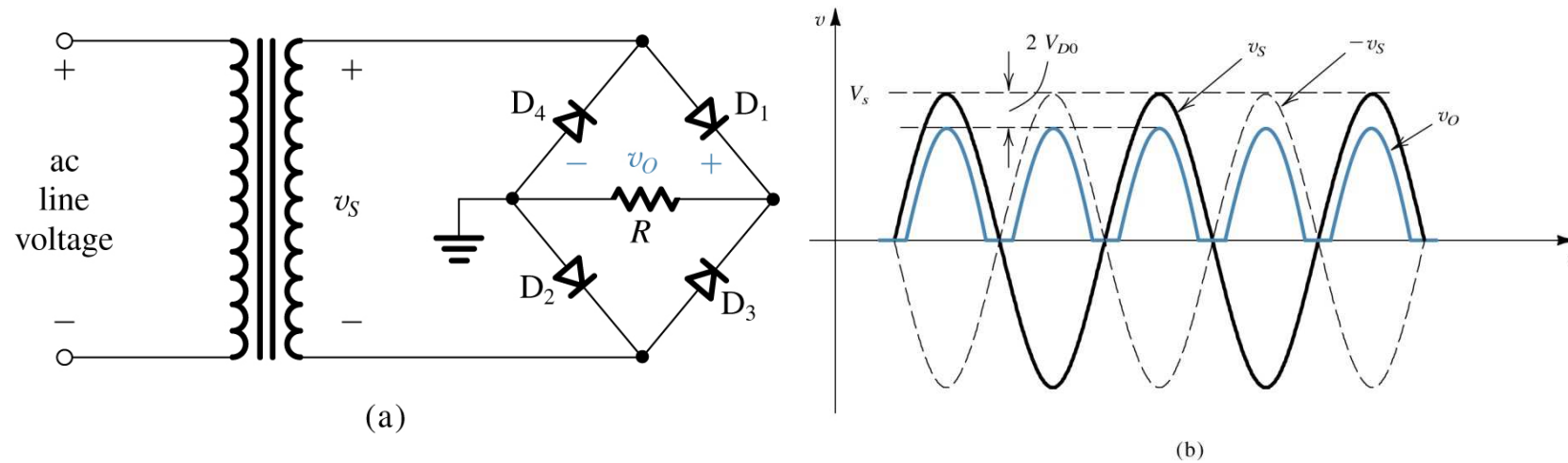

# PIV for the Bridge Rectifier

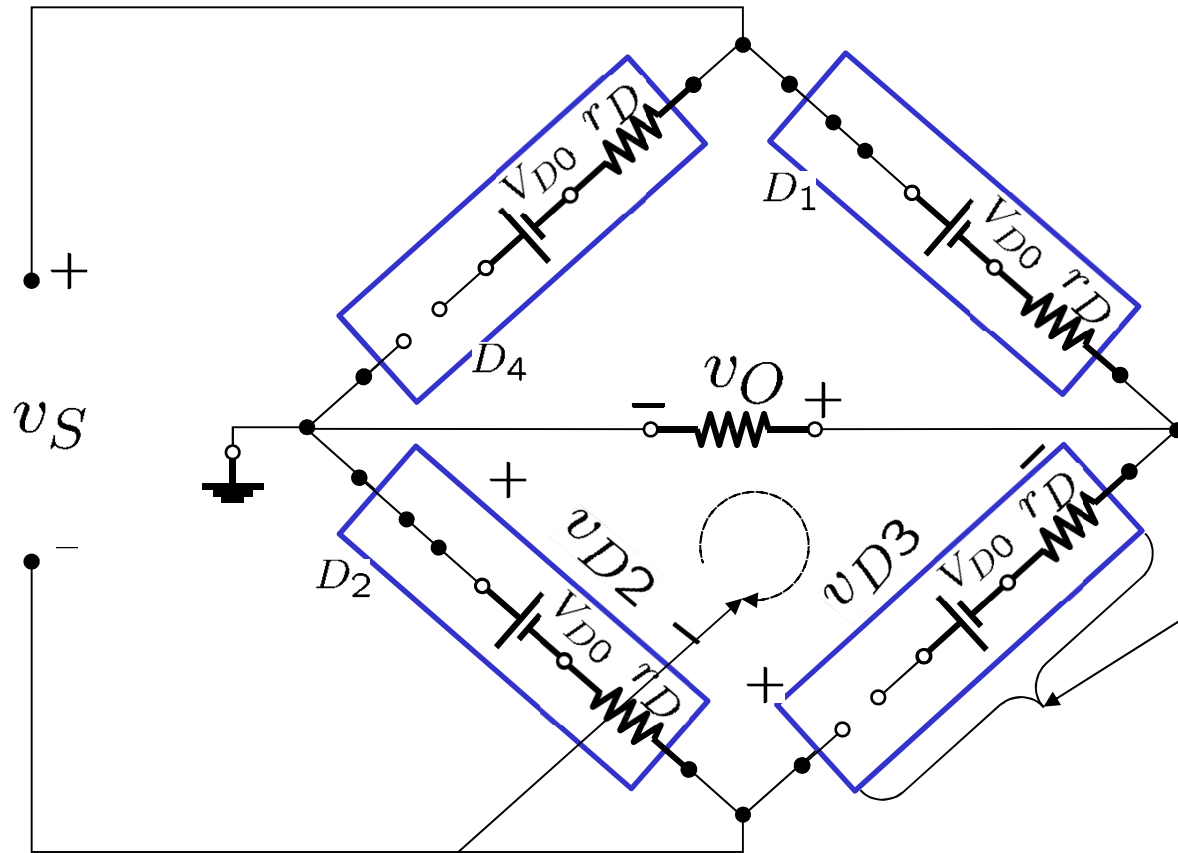

Consider this diode in the reverse-region



To avoid breakdown, we need to know the maximum negative voltage that  $v_{D3}$  can experience

**KVL**  $\rightarrow v_{D3} = -(v_{D2} + v_O)$


Since  $r_D \ll \rightarrow v_{D2} \approx V_{D0}$

Also  $v_O \approx (v_S - 2V_{D0})$  **Hence**  $v_{D3} = -v_S + V_{D0}$


# PIV for the Bridge Rectifier

$$v_{D3} = -v_S + V_{D0}$$

Becomes the lowest negative, when

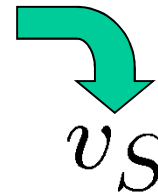

reaches its maximum or peak value of

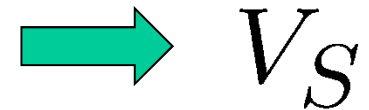

$$v_{D3\min} = -V_S + V_{D0}$$

**Hence,**

$$\text{PIV} = |v_{D3\min}| = V_S - V_{D0}$$

## Comparison Between Rectifiers in terms of their PIV voltages

$$\text{PIV}_{(\text{One-diode Half-Wave})} = V_S$$

$$\text{PIV}_{(\text{Two-diode Full-Wave})} = 2V_S - V_{DO} \quad \text{Worst}$$


$$\text{PIV}_{(\text{Bridge rectifier})} = V_S - V_{DO} \quad \text{Better}$$

# The Half-Wave Peak Rectifier

$$i_L = \frac{V_0}{R}$$

$$i_D = i_C + i_L$$

$$i_D = C \frac{dv_I}{dt} + i_L$$

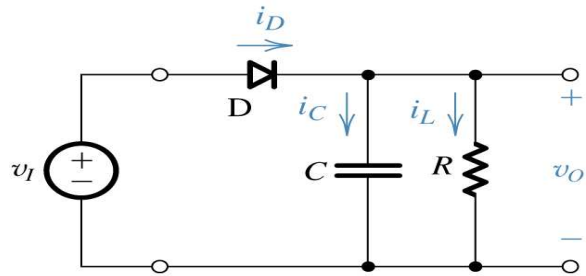

(a)

$$V_p - V_r = V_p e^{-T/RC}$$


$$V_r \approx V_p \frac{T}{RC}$$

$$V_r = \frac{V_p}{fCR}$$


$$I_L = \frac{V_p}{R}$$

$$V_o = V_p - \frac{1}{2} V_r$$

$$v_o = V_p e^{-t/CR}$$

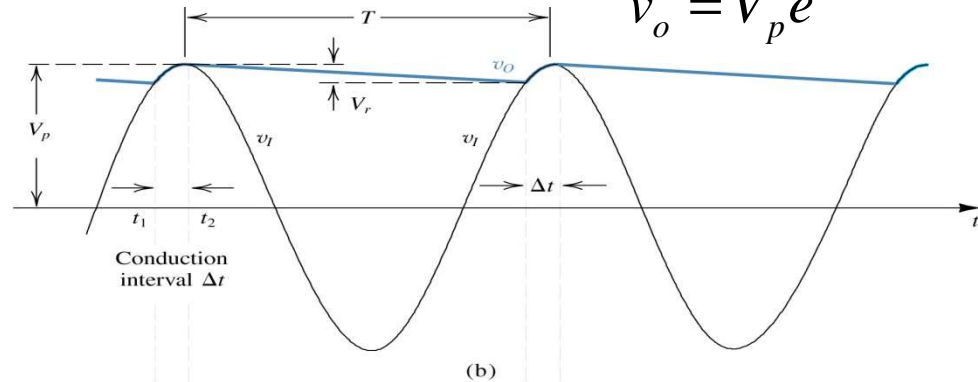

(b)

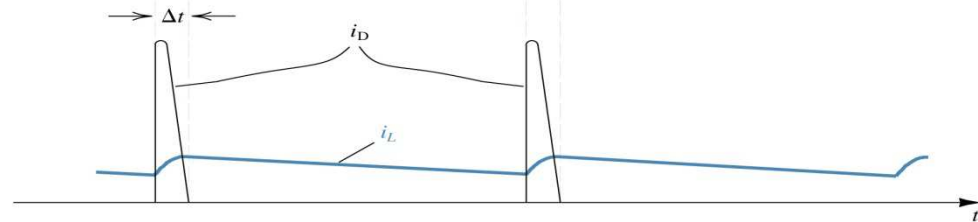


(c)

$$i_{D\text{av}} = I_L \left( 1 + \pi \sqrt{2V_p / V_r} \right)$$

$$i_{D\text{max}} = I_L \left( 1 + 2\pi \sqrt{2V_p^{1.3} / V_r} \right)$$

$$v_O = V_p e^{-t/RC}$$

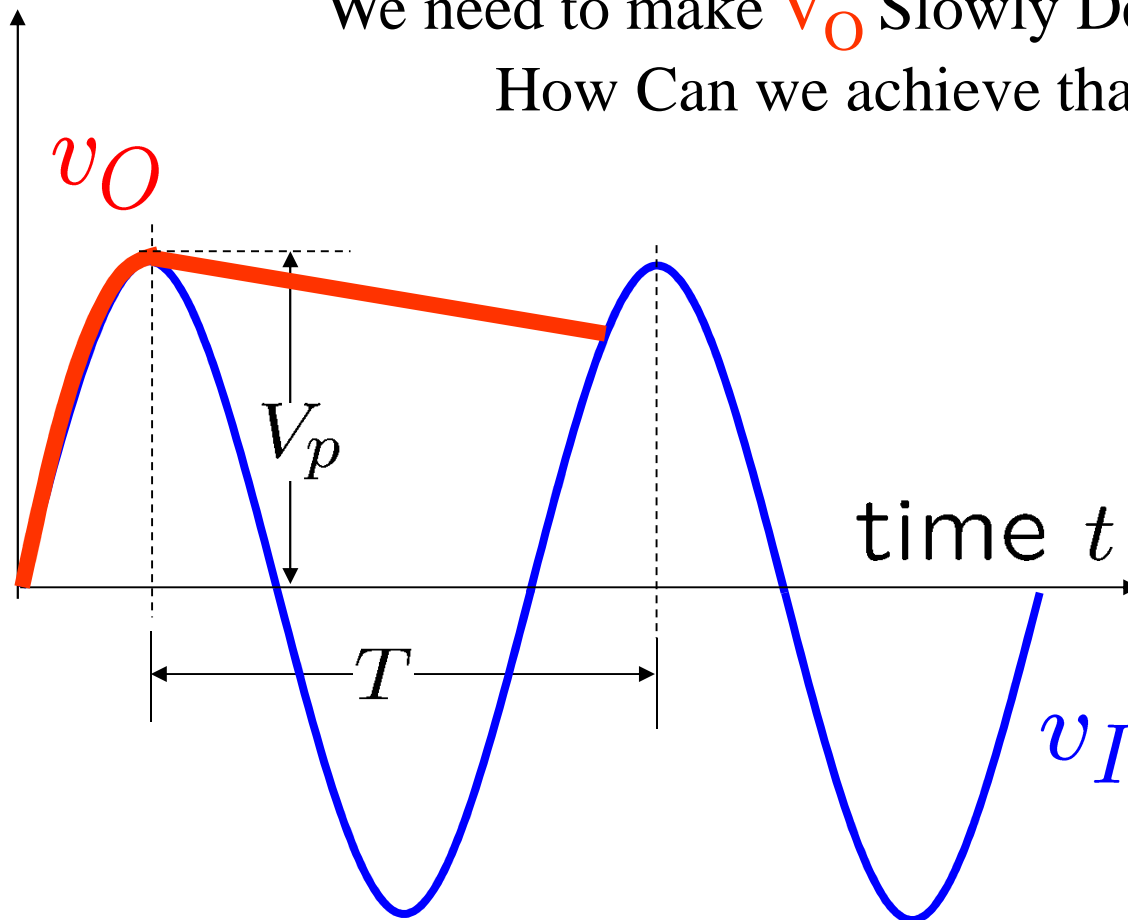
We need to make  $v_O$  Slowly Decaying,  
How Can we achieve that?




We can choose

$$RC \gg T \rightarrow$$

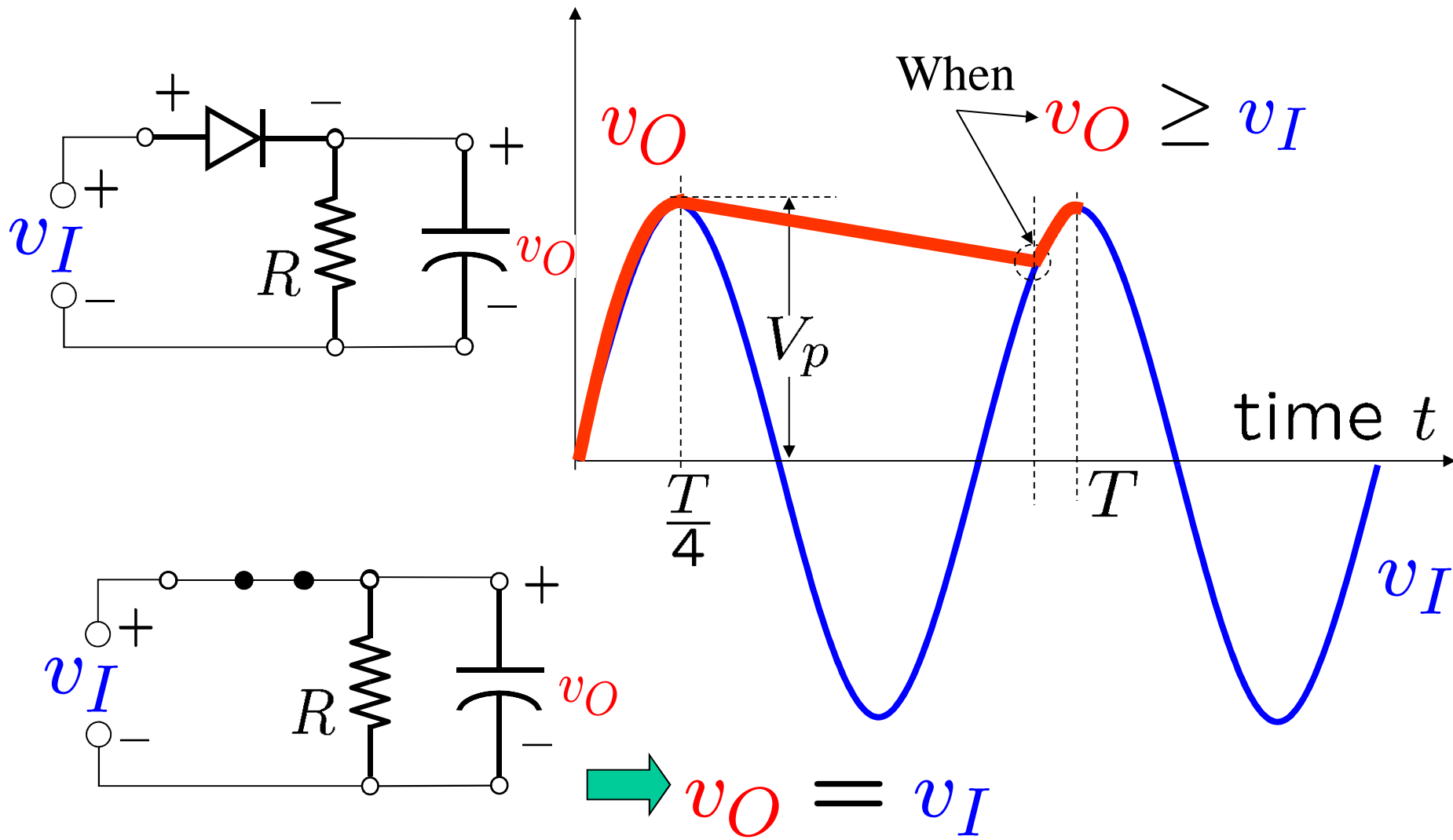
This will make  
the discharge time  
longer and the  
output  
voltage will not  
decay quickly



The picture in steady-state

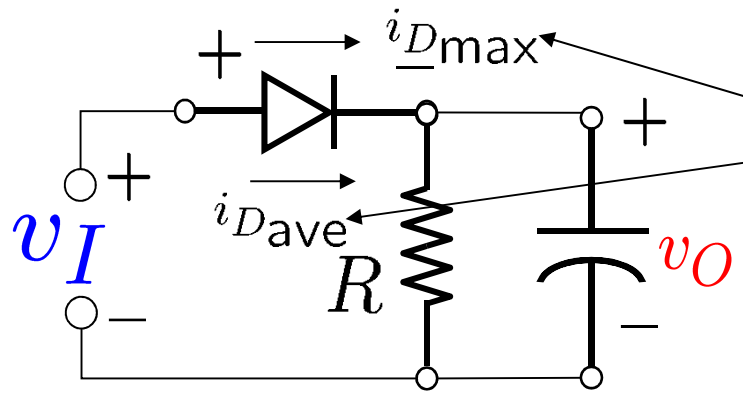


We need to calculate those values

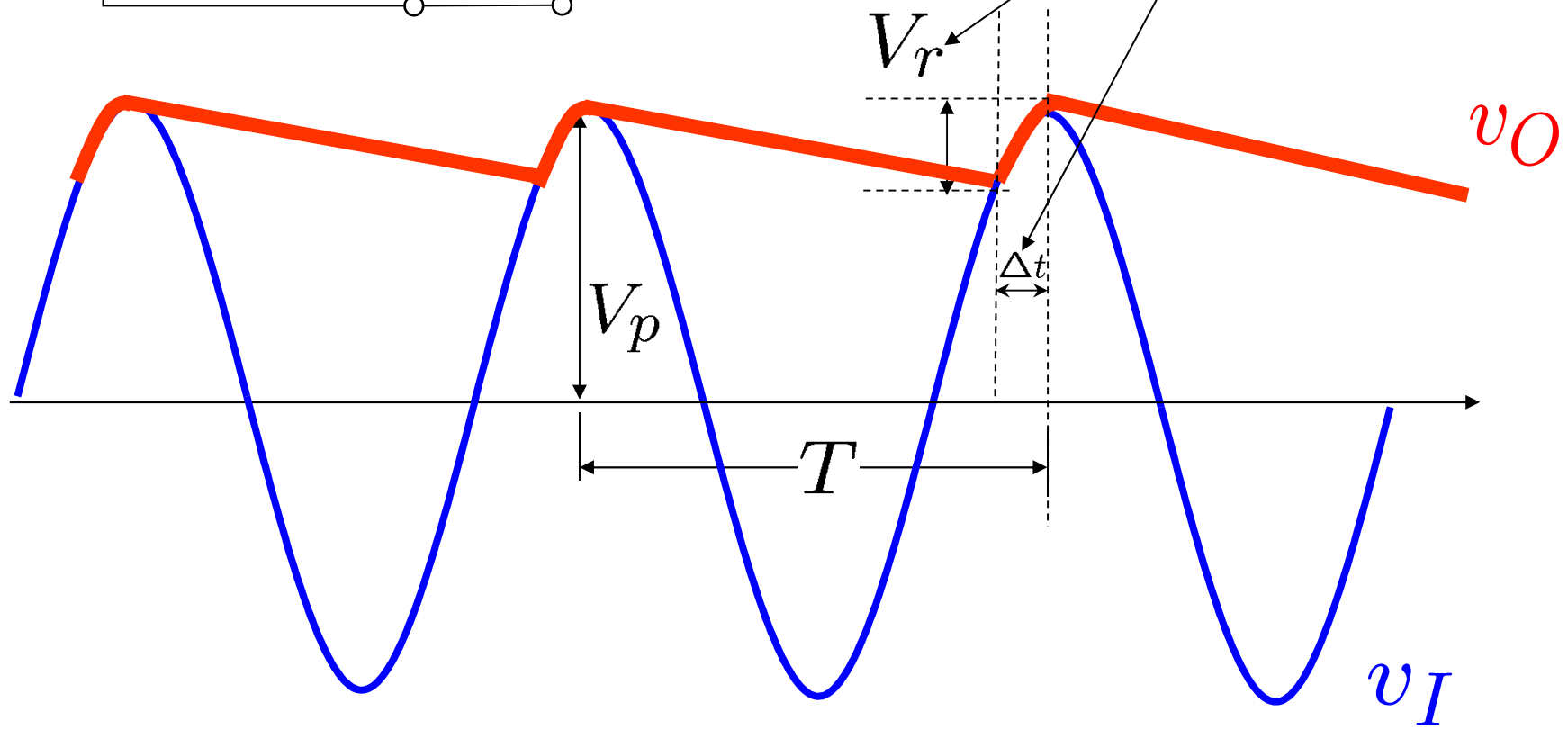


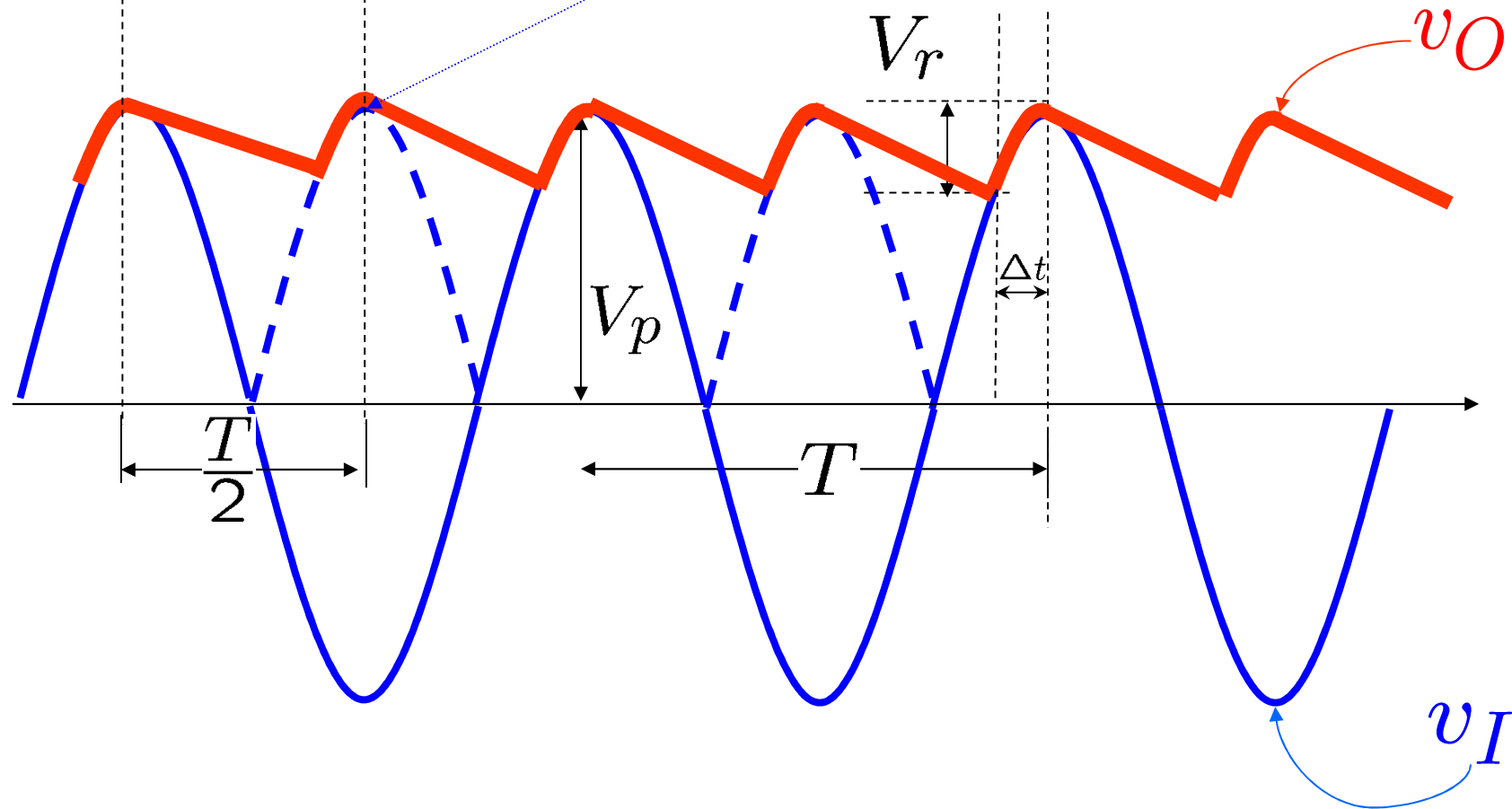
# The picture at Steady-State

As if the output is following the peak of the shadow of negative cycle in the input waveform



# Full-Wave Peak Rectifier Ideal Diodes

Half-wave Peak Rectifier

$$V_r = \frac{V_p T}{RC} = \frac{V_p}{fRC}$$

$$\omega \Delta t \simeq \sqrt{(2V_r/V_p)}$$

$$i_{D\text{ave}} = I_L(1 + \pi\sqrt{2V_p/V_r})$$

$$i_{D\text{max}} = I_L(1 + 2\pi\sqrt{2V_p/V_r})$$

Gets halved

Same

Same

Same

Full-wave Peak Rectifier

$$V_r = \frac{V_p T}{2RC} = \frac{V_p}{2fRC}$$

$$\omega \Delta t \simeq \sqrt{(2V_r/V_p)}$$

$$i_{D\text{ave}} = I_L(1 + \pi\sqrt{2V_p/V_r})$$

$$i_{D\text{max}} = I_L(1 + 2\pi\sqrt{2V_p/V_r})$$

