 


# Field-Effect Transistors



The **field-effect transistor (JFET)** is the simplest type of field effect transistors.

- Structure
- Current-voltage Characteristics
- MOSFET as an Amplifier
- CMOS
- The CMOS Digital Logic Inverter



  
# n-channel Enhancement mode MOSFET

Two n-regions called **source** terminal and **drain** terminal. The current in a MOSFET is the result of flow of charge in the inversion layer called the channel region.



For  $v_{DS} \ll$

 

The channel width is uniform


# $i_D - v_{DS}$ Characteristics

**Cutoff; Triode (switch); and Saturation (amplifier) regions**


$v_{GS} \geq V_t$  (Induced Channel)

$$V_t = 1 \text{ V}$$
 
$$k'_n \left( \frac{W}{L} \right) = 0.5 \text{ mA/V}^2$$



(a)

 

To operate the MOSFET in the **triode** region

$$v_{DS} < v_{GS} - V_t$$
$$i_D = k'_n \frac{W}{L} \left[ (v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

$$i_D = k'_n \frac{W}{L} (v_{GS} - V_t) v_{DS}$$

$$r_{DS} = \frac{v_{DS}}{i_D} = \left[ k'_n \frac{W}{L} (v_{GS} - V_t) \right]^{-1}$$

# To operate the MOSFET in the saturation region

$i_D - v_{GS}$  Characteristics

for an enhancement - type NMOS transistor in Saturation

( $V_t = 1\text{ V}$ ,  $k'_n W/L = 0.5\text{ mA/V}^2$ )

$$v_{GS} \geq V_t$$


$$v_{GD} \leq V_t$$

$$v_{DS} \geq v_{GS} - V_t$$


$$v_{DS} = v_{GS} - V_t$$

$$i_D = \frac{1}{2} k'_n \frac{W}{L} v_{DS}^2$$

 
$$i_D = \frac{1}{2} k'_n \frac{W}{L} v_{DS}^2$$



 $i_D$ - $v_{GS}$  characteristics for an enhancement-type NMOS transistor in Saturation ( $V_t = 1$  V,  $k'_n W/L = 0.5$  mA/V<sup>2</sup>)




 Increasing  $v_{DS}$  beyond  $v_{DSsat}$  causes the channel pinch-off to move away from the drain.





 
## Effect of $v_{DS}$ on $i_D$ in the saturation region




 Large-signal equivalent circuit model of the **n**-channel MOSFET in saturation.





 
## Exercise 5.3

- An Enhancement-type NMOS transistor with  $V_t = 2$  V has its source terminal grounded and a 3-V DC source connected to the gate. In what region of operation does the device operate for:
  - $V_D = +0.5$  V ( $v_{DS} \leq v_{GS} - V_t$ : Triode)
  - $V_D = 1$  V ( $v_{DS} \geq v_{GS} - V_t$ : Saturation)
  - $V_D = 5$  V ( $v_{DS} \geq v_{GS} - V_t$ : Saturation)


   
# The Current-Voltage Characteristics of the Depletion n-Channel MOSFET for Which $V_t = -4\text{V}$ and $k'_n W/L = 2 \text{ mA/V}^2$



# The MOSFET as an Amplifier


## DC Bias

$$I_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_t)^2$$

$$V_D = V_{DD} - R_D I_D$$

To Ensure Saturation

$$V_D \gg V_{GS} - V_t$$

 

# The Signal Current in the Drain Terminal


$$v_{GS} = V_{GS} + v_{gs}$$


$$i_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} + v_{gs} - V_t)^2$$

$$i_D = I_D + i_d$$


$$i_d = k'_n \frac{W}{L} (V_{GS} - V_t) v_{gs}$$
 
$$g_m = \frac{i_d}{v_{gs}} = k'_n \frac{W}{L} (V_{GS} - V_t)$$



 




# Small Signal Equivalent Circuit

 



# The T Model

 

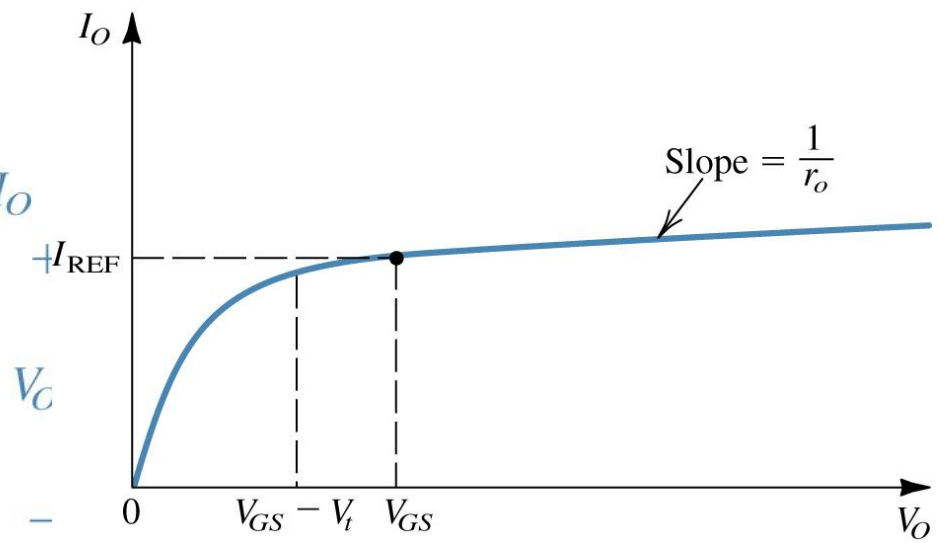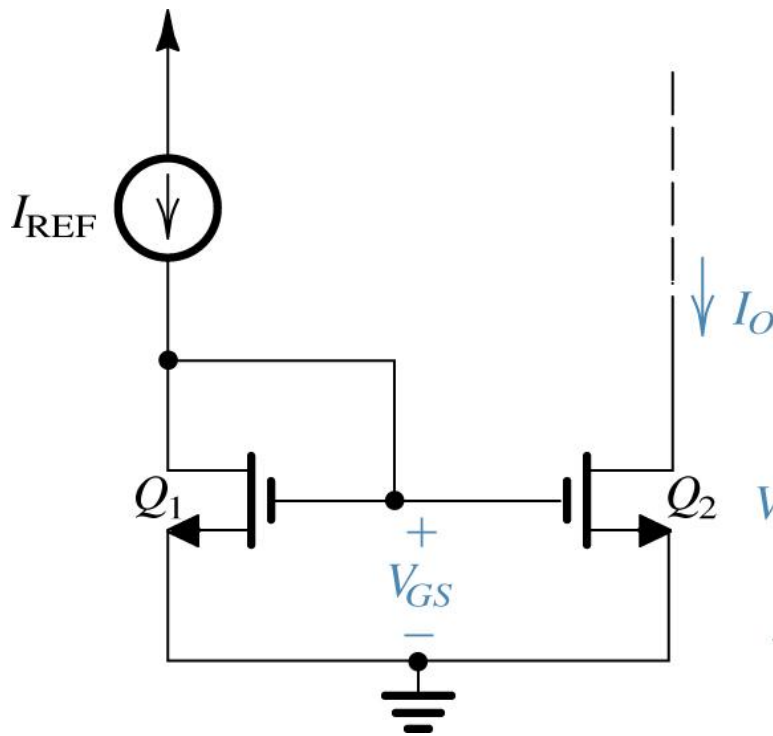


# Basic Configurations of Single-Stage IC MOS Amplifiers

- Common Source (CS)
- Common Gate (CG)
- Common Drain (CD)


# CMOS Common-Source Amplifier

$$r_{o2} = \frac{|V_{A2}|}{I_{REF}}$$

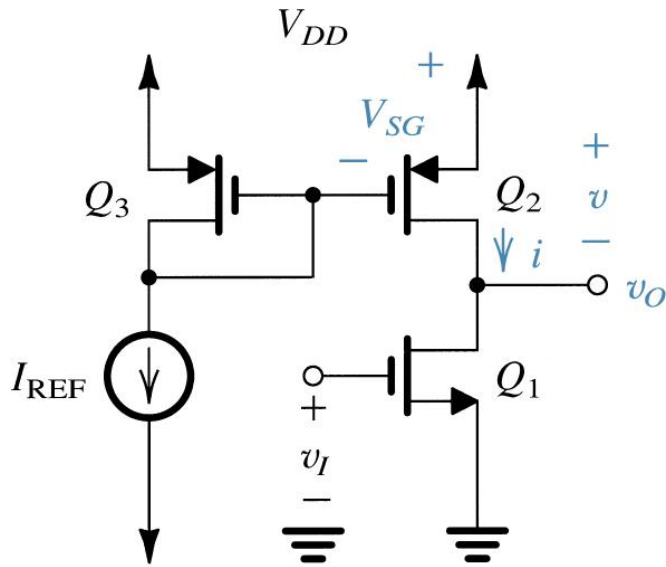
$$A_v = \frac{v_o}{v_i} = -g_m (r_{o1} // r_{o2})$$



(a)

 

(d)



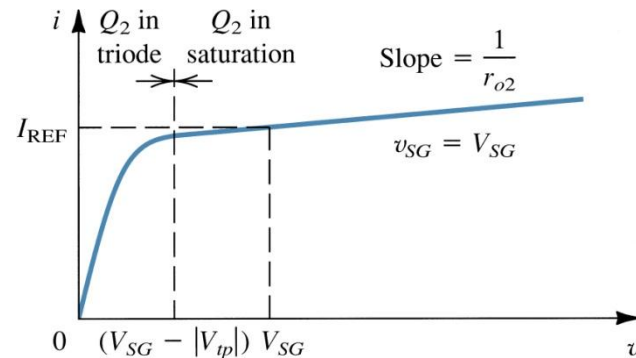


# The CMOS Common - Gate Amplifier


$$A_v = \frac{v_o}{v_i} = \left( g_{m1} + g_{mb1} + \frac{1}{r_{o1}} \right) (r_o // r_{o2})$$

$$A_v \cong (g_{m1} + g_{mb1}) (r_{o1} // r_{o2})$$
 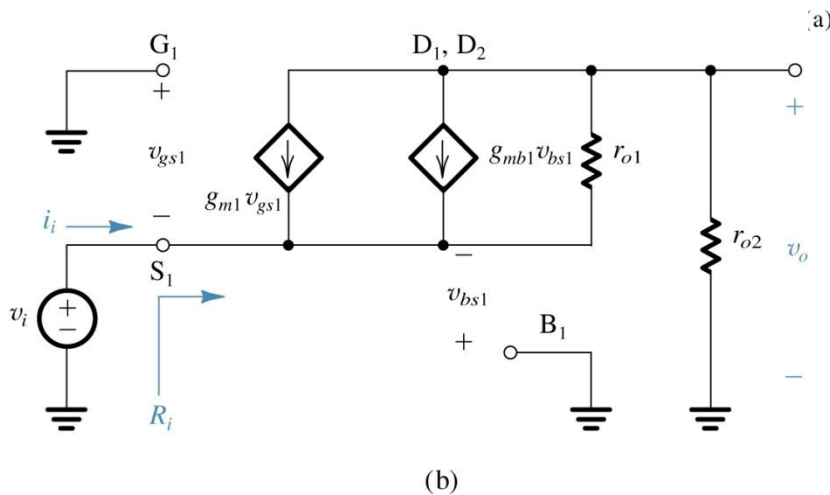 
$$R_i \cong \frac{v_i}{i_i} \approx \frac{1}{(g_{m1} + g_{mb1})} \left( 1 + \frac{r_{o2}}{r_{o1}} \right)$$


 
# The Common-Drain or Source-Follower Amplifier




(a)


$$A_v = \frac{v_o}{v_i} = \frac{g_{m1} R_S}{1 + g_{m1} R_S}$$

$$A_v = \frac{g_{m1}}{g_{m1} + g_{mb1} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}} = \frac{g_{m1}}{g_{m1} + g_{mb1}}$$
 
$$R_o = (1/g_{m1}) \parallel (1/g_{mb1}) \parallel r_{o1} \parallel r_{o2}$$





(b)



 


(c)

# NMOS Amplifier with Enhancement Load

 
 


# The NMOS Amplifier with Depletion Load

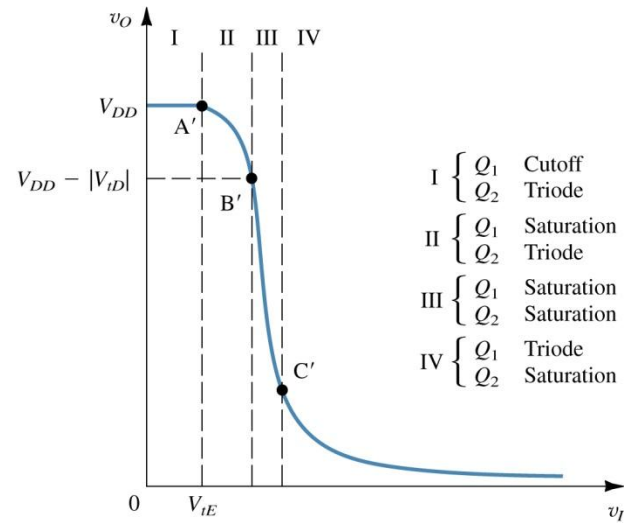 
 




# CMOS Inverter

  


 
 
# Operation of the CMOS Inverter When $v_I$ is High



$$r_{DS} = 1 / \left[ k'_n \left( \frac{W}{L} \right)_n (V_{DD} - V_{tn}) \right]$$


(c)
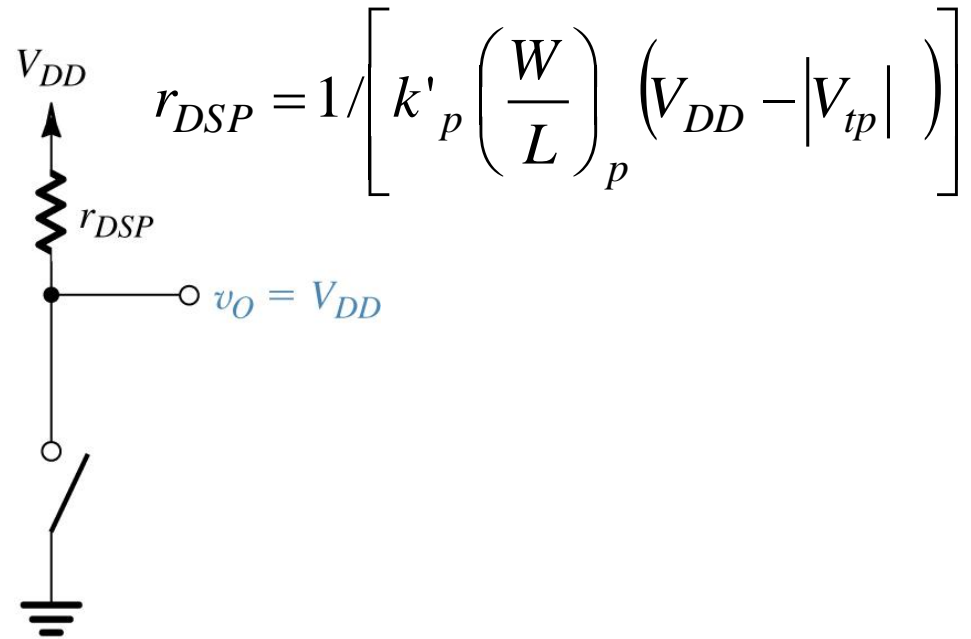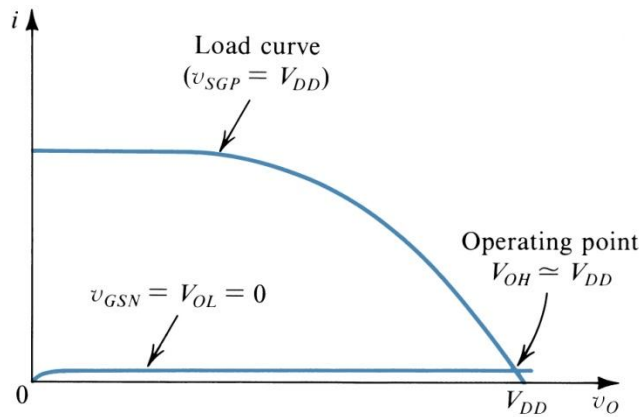 
# Operation of the CMOS Inverter When $v_I$ is Low



(c)
 
# The Voltage Transfer Characteristics of the CMOS Inverter and Noise Figures



$$V_{IH} = \frac{1}{8}(5V_{DD} - 2V_t)$$

$$V_{IL} = \frac{1}{8}(3V_{DD} + 2V_t)$$


$$N_{MH} = V_{OH} - V_{IH}$$

$$N_{ML} = V_{IL} - V_{OL}$$

$$V_{th} = \frac{r(V_{DD} - |V_{tp}|) + V_{th}}{1 + r}$$

$$r = \sqrt{\frac{k'_p (W/L)_p}{k'_n (W/L)_n}}$$




# Dynamic Operation

 

$$t_{PHL} = \frac{1.6C}{k'_n (W/L)_n V_{DD}} \text{ (High to Low)}$$

$$t_{PLH} = \frac{1.6C}{k'_p (W/L)_p V_{DD}} \text{ (Low to High)}$$
   
$$t_p = \frac{t_{PHL} + t_{PLH}}{2} \text{ (Propagation Delay)}$$



(d)