

ELG2331: DGD Chapters 3, 4, 5, and 7

Problem 3.5

At node 1

$$\frac{v_1}{200} + \frac{v_1 - v_2}{5} + \frac{v_1 - v_3}{100} = 0$$

At node 2

$$\frac{v_2 - v_1}{5} + i + 0.2 = 0$$

At node 3

$$-i + \frac{v_3 - v_1}{100} + \frac{v_3}{50} = 0$$

We have also

$$v_3 - v_2 = 50 \text{ V}$$

After solving these equations, we obtain:


$$v_1 = -45.53 \text{ V}$$

$$v_2 = -48.69 \text{ V}$$

$$v_3 = 1.31 \text{ V}$$

$$i = 491 \text{ mA}$$

Problem 3.19

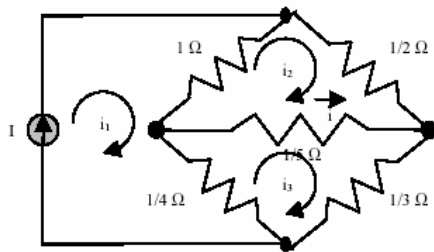

Mesh 1:

$$i_1 = I$$

Mesh 2:

$$i_1(-1) + i_2\left(1 + \frac{1}{2} + \frac{1}{5}\right) + i_3\left(-\frac{1}{5}\right)$$

Mesh 3:

$$i_1\left(-\frac{1}{4}\right) + i_2\left(-\frac{1}{5}\right) + i_3\left(\frac{1}{4} + \frac{1}{3} + \frac{1}{5}\right) = 0$$

Solve these equations to obtain

$$i_2 = 0.65 I$$

$$i_3 = 0.48 I$$

$$i = i_3 - i_2 = 0.48 I - 0.65 I = -0.16 I$$

Problem 4.48

Apply current divider

$$I_R = I_S \frac{\frac{1}{R}}{\frac{1}{R} + \frac{1}{Z_C}} = 157 \angle 99.04^\circ \text{ mA}$$

$$i_R(t) = 157 \cos(200\pi t + 99.04^\circ) \text{ mA}$$

Problem 4.68

$$\frac{V_0 - 0}{Z_{R_L}} + \frac{V_0 - 0}{Z_C} + \frac{V - V_i}{Z_L} = 0$$

$$V_i = 4 \angle 30^\circ \text{ V}$$

$$Z_C = 80 \angle -90^\circ$$

$$Z_L = 60 \angle 90^\circ$$

$$V_0 = 7.155 \angle -33.43^\circ$$

$$v_0(t) = 7.155 \cos(\omega t - 33.43^\circ)$$

Problem 5.24

Apply KCL:

$$i_C(0^-) = 0; V_C(0^-) = 0$$

$$V_C(0^-) = V_C(0^+)$$

At this moment the capacitor will be acting as a DC source but with zero voltage (short circuit)

Therefore all voltage V_1 will appear across R_1 and the current through R_1 is the current through the capacitor

$$i_C(0^+) + \frac{V_C(0^+)}{R_2} + \frac{V_C(0^+)}{R_1} = 0$$

$$i_C(0^+) = \frac{V_1}{R_1} = \frac{12}{400 \times 10^{-3}} = 30 \text{ A (when the switch is closed)}$$

Problem 5.26Apply KVL (At $t = 0^-$):

$$-V_S + i_L(0^-)R_S + V_L(0^-) = 0$$

$$i_L(0^-) = \frac{V_S}{R_S} = \frac{12}{0.7} = 17.14$$

Apply KVL (At $t = 0^+$):

$$i_L(0+)R_1 + V_L(0+) = 0$$

$$V_L(0+) = -i_L(0+)R_1 = -17.14 \times 22 \times 10^3 = -337.1 \text{ kV}$$

Problem 7.17:

The apparent power is

$$S = \frac{\tilde{V}^2}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} = \frac{50^2}{\sqrt{20^2 + 26.5^2}} = 75.3 \text{ VA}$$

The real power is

$$P = S \cdot \cos \theta = 75.3 \times \frac{20}{33.2} = 45.36 \text{ W}$$


The reactive power is

$$Q = \sqrt{S^2 - P^2} = \sqrt{75.3^2 - 45.36^2} = -60 \text{ VAR}$$

The angle is


$$\theta = \cos^{-1}\left(\frac{R}{Z}\right) = 53^\circ$$

The power triangle is shown

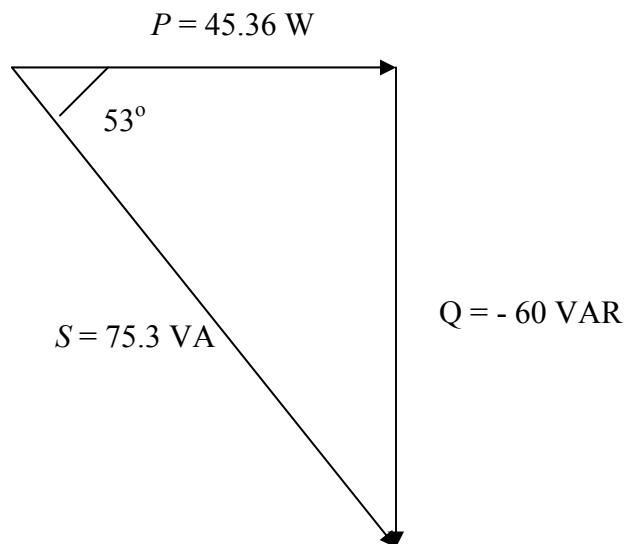

Problem 7.21

a) The equivalent circuit is:

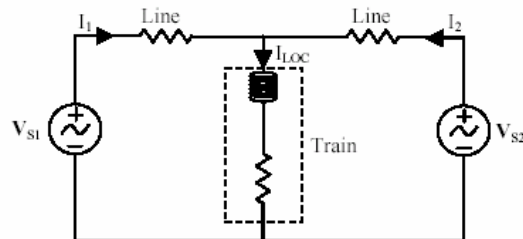

b) The locomotive current for the 10% voltage drop is:

$$I_{LOC} = I_1 + I_2 = 2I_1 = 2I_2 = \frac{P_{LOC}}{(V_S - 10\%)\cos(\theta)} = \frac{11 \text{ MW}}{22.5 \text{ kV} \times 0.8} = 611 \text{ A}$$

c) The reactive power is:

$$Q = \sqrt{S_{LOC}^2 - P_{LOC}^2} = \sqrt{(V_S - 10\%)^2 I_{LOC}^2 - P_{LOC}^2} = \sqrt{(13.75)^2 - (11)^2} = 8.25 \text{ MVAR}$$

d) The supplied real power is:

$$P = \sqrt{S^2 - Q^2} = \sqrt{(V_S \cdot I)^2 - Q^2} = 12.85 \text{ MW}$$

The over-head line power loss is:

$$P_{line} = -P_{LOC} + \sqrt{(V_S \cdot I)^2 - Q^2} = -11 + \sqrt{(15.27)^2 - (8.25)^2} = 1.85 \text{ MW}$$

The maximum distance between the two power stations is:

$$R_{Line} // R_{Line} = \frac{P_{Line}}{I_{LOC}^2} = 5 \Omega$$

$$\text{Distance}_{\max} = \frac{2 R_{Line}}{0.2 \Omega/\text{km}} = 100 \text{ km}$$

e) The over-head line power loss is:

$$P_{LOC} = 10\% V_S \cdot I_{LOC} \cdot \cos(\theta) = 2500 \text{ V} \times 489 \text{ A} = 1.22 \text{ MW}$$

f) The over-head line power loss is:

$$I_{LOC} = \frac{0.25P_{LOC}}{90\% \times V_{S,DC}} = \frac{2.75}{1350} = 2037 \text{ A}$$

$$P_{Line} = 10\% \times V_{S,DC} \times I_{LOC} = 305 \text{ kW}$$

$$R_{Line} // R_{Line} = \frac{P_{Line}}{I_{LOC}^2} = 0.0735 \Omega$$

$$\text{Distance}_{\max} = \frac{2R_{Line}}{0.2\Omega/\text{km}} = 1.5 \text{ km}$$

Problem 7.26

$$Z = 7 \angle 10^0 \Omega = 6.89 + j1.21 \Omega$$

$$Z_{eq} = \frac{ZZ_C}{Z + Z_C} = \frac{(R + jX)(-jX_C)}{(R + jX) + (-jX_C)} = \frac{XX_C - jRX_C}{R + j(X - X_C)} \frac{R - j(X - X_C)}{R - j(X - X_C)}$$

$$= \frac{(XX_C R - RX_C(X - X_C)) - j(R^2 X_C - XX_C(X - X_C))}{R^2 + (X - X_C)^2} = R_{eq} - jX_{eq}$$

$$I_S = \frac{V_0}{Z_{eq}}$$

$$Z_{eq} = R_{eq} - jX_{eq} = R_{eq} - 0$$

$$X_{eq} = 0$$

$$R^2 X_C - XX_C(X - X_C) = 0$$

$$XC = \frac{R^2 + X^2}{X} = 40.31 \Omega = \frac{1}{\omega C}$$

$$C = \frac{1}{\omega X_C} = \frac{1}{377 \times 40.31} = 65.8 \mu F$$