

**ELG2331: Experiment 5**  
**Simulation of Shunt-Connected DC Motor**  
**Based on P19.36 and P19.38 Textbook 5<sup>th</sup> Edition**

**Part 1**

Derive the differential equations describing the electrical and mechanical dynamics of a shunt-connected DC motor. And draw a simulation block diagram of the system. The motor parameters are  $k_a$ ,  $k_T$  = armature and torque reluctance constant and  $k_f$  = field flux constant.

**Part 2**

Develop a Simulink simulator for the above shunt-connected DC motor. Assume the following parameter values:  $L_a = 0.15$  H;  $L_f = 0.05$  H;  $R_a = 1.8$   $\Omega$ ,  $R_f = 0.2$   $\Omega$ ;  $k_a = 0.8$  V-s/rad;  $k_T = 20$  N-m/A;  $k_f = 0.02$  Wb/A;  $b = 0.1$  N-m-s/rad;  $J = 1$  kg-m<sup>2</sup>.

**See Figure P19.36 (5<sup>th</sup> edition) or Figure P17.35 (4<sup>th</sup> edition)**