


# **Bipolar Junction Transistors (BJT)**

Signal amplification is important in many applications, such as telecommunications. Before the advent of transistors, signal amplification was accomplished using vacuum tubes. Transistors are much smaller and do not need a long warm-up time needed with vacuum tubes. The invention of the bipolar junction transistor started a revolution which placed electronics on a path of miniaturization; a fact that would have been impossible with vacuum tubes.

**In summary, the transistor and subsequently the integrated circuit must certainly qualify as two of the greatest inventions of the twentieth century.**
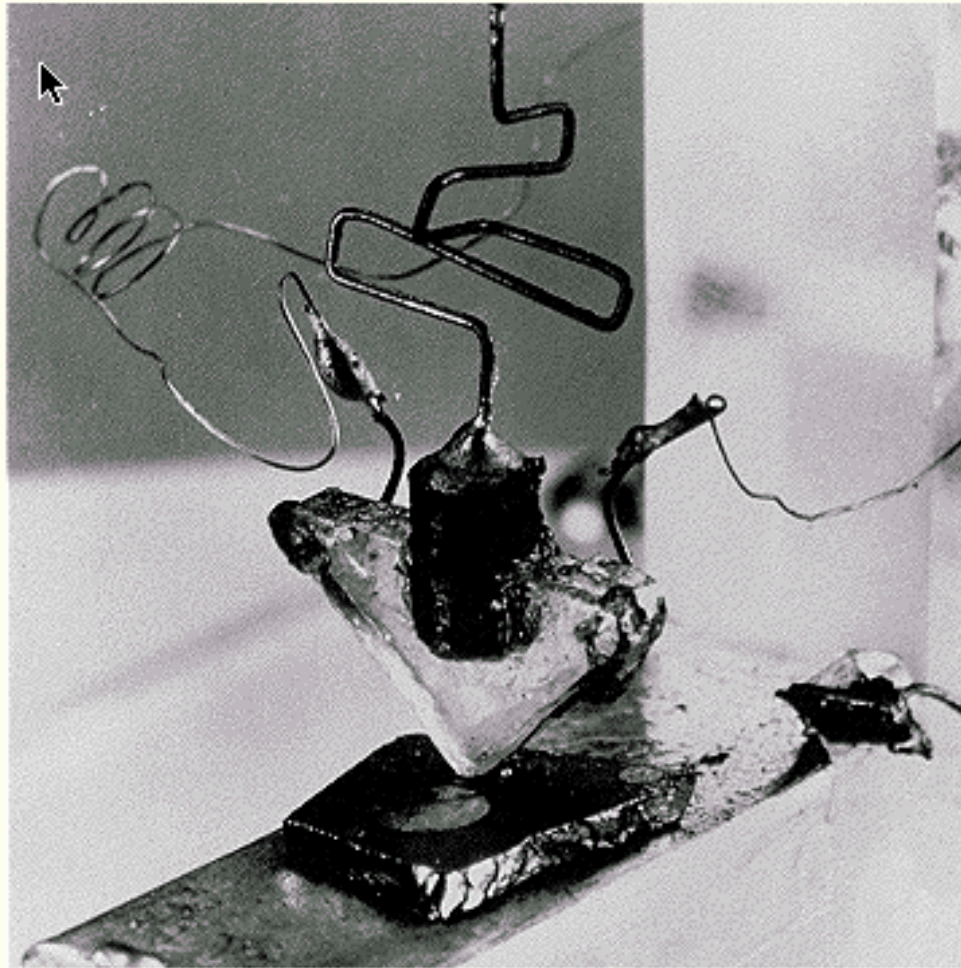
# The First Transistor


Dr. Lindsey Archive <http://www.cs.colorado.edu/~lindsay/index.html>


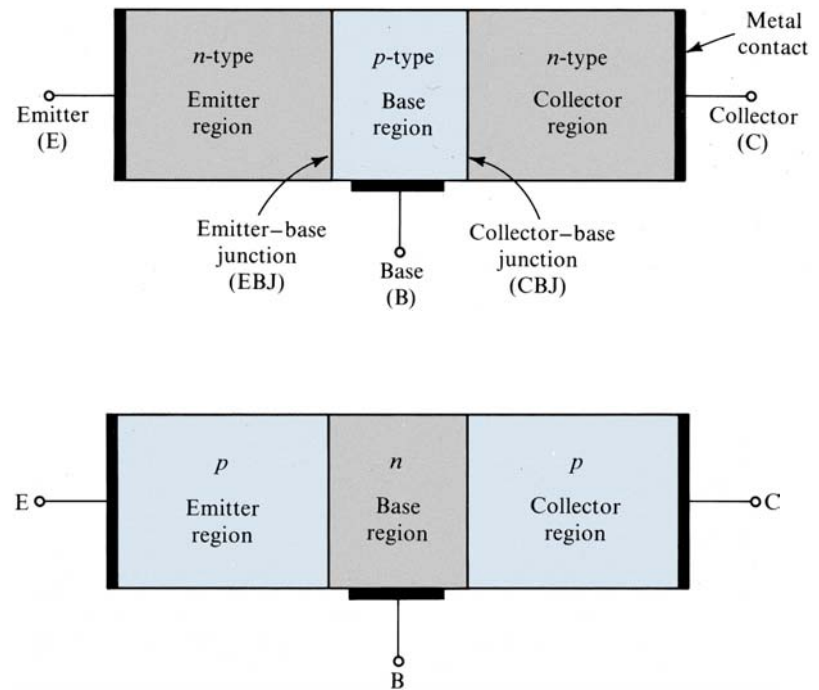
# BJT Structure

By placing two PN junctions together we can create a bipolar transistor. A BJT transistor has three terminals. The base (B), the collector (C), and the emitter (E).

- Transistors are three-terminal devices. The terminals are labelled the base, the emitter and the collector. Each BJT consists of two  $pn$  junctions (where a 'p type' material joins to a 'n type material'). Therefore, a transistor may be made up from a piece of  $p$  type material sandwiched between two  $n$  type regions ( $nnp$ ), or it may be made up from a piece of 'n type' material sandwiched between two 'p type' regions ( $pnnp$ )




# The Transistor as an Amplifier: DC Condition

The transistor should be in the active region. Biasing means establishing a constant DC current in the emitter or the collector. The operation of the transistor as an amplifier is highly influenced by the value of the quiescent (bias) current.


$$I_E = I_C / \alpha$$

$$I_B = I_C / \beta$$

$$V_C = V_{CE} = V_{CC} - I_C R_C$$

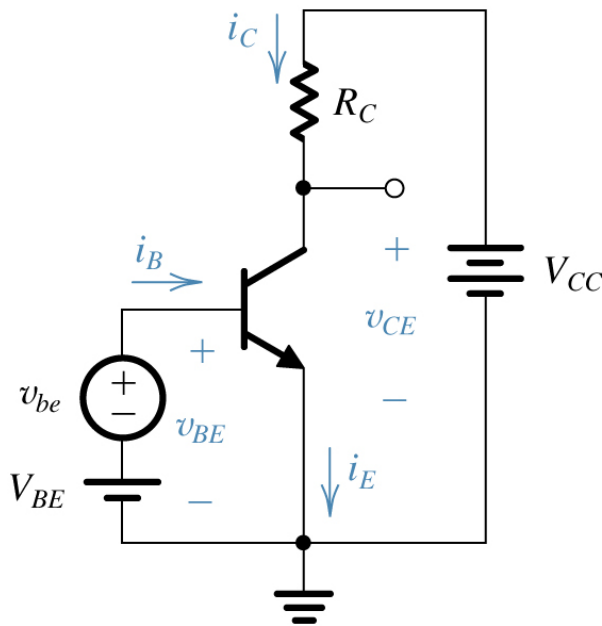


(a)

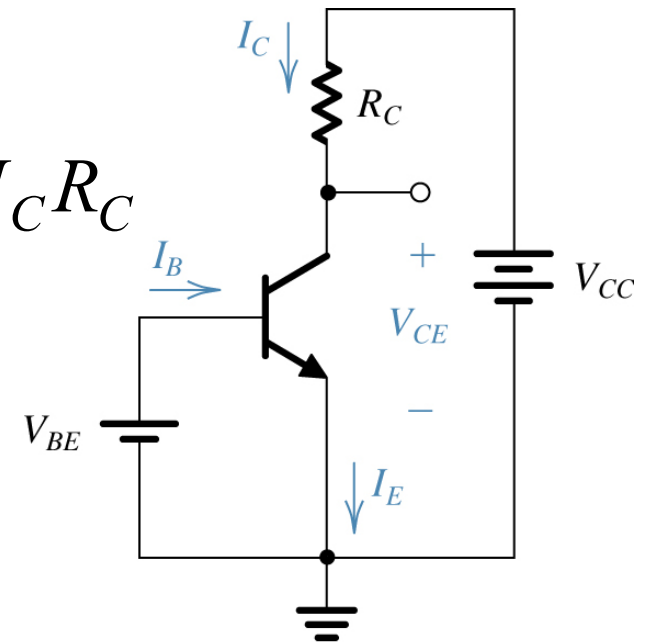


(b)
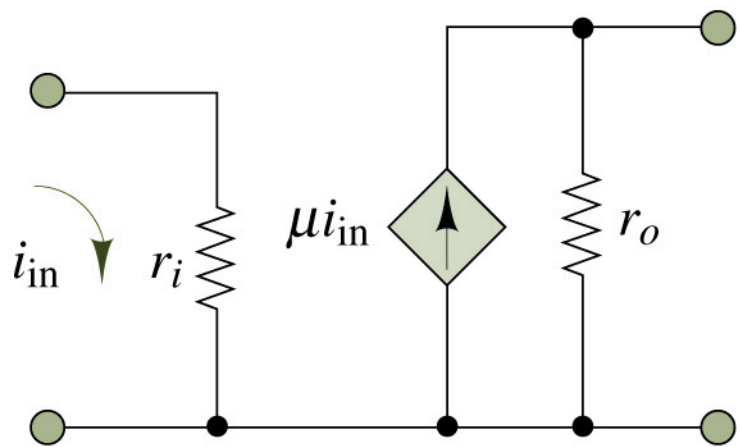
# Controlled-Source Models of Linear Amplifier Transistor Operation


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




(a) Current-controlled current source

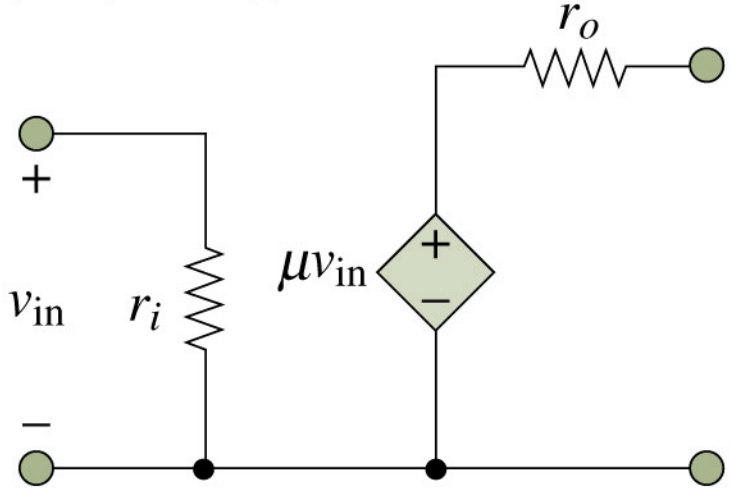

(b) Voltage-controlled voltage source

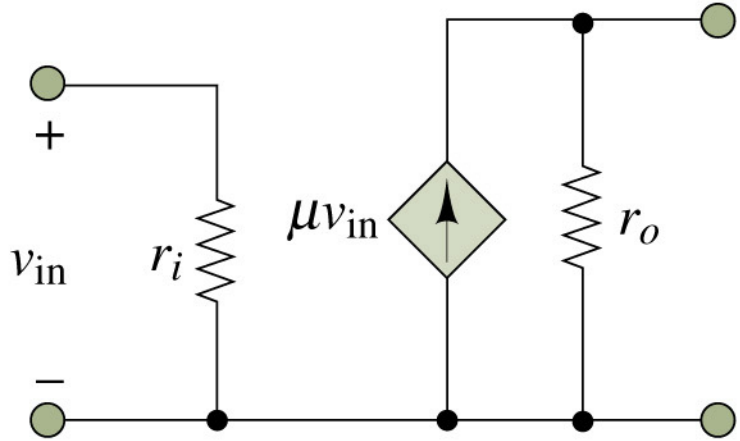


(c) Voltage-controlled current source

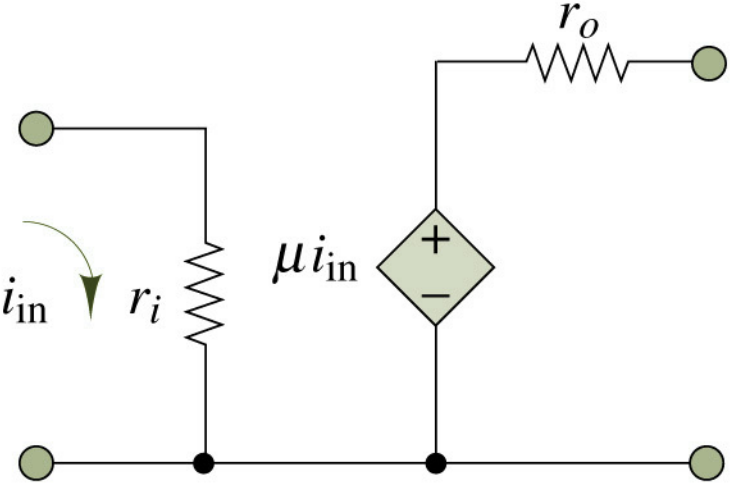


(d) Current-controlled voltage source
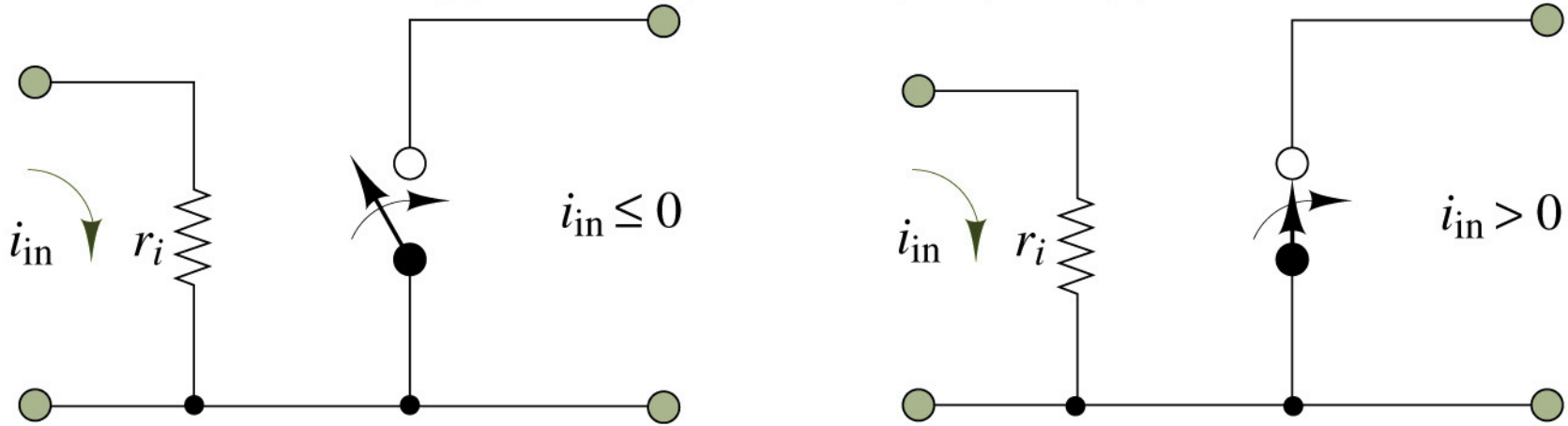
# Models of Ideal Transistor Switches

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Current-controlled switch

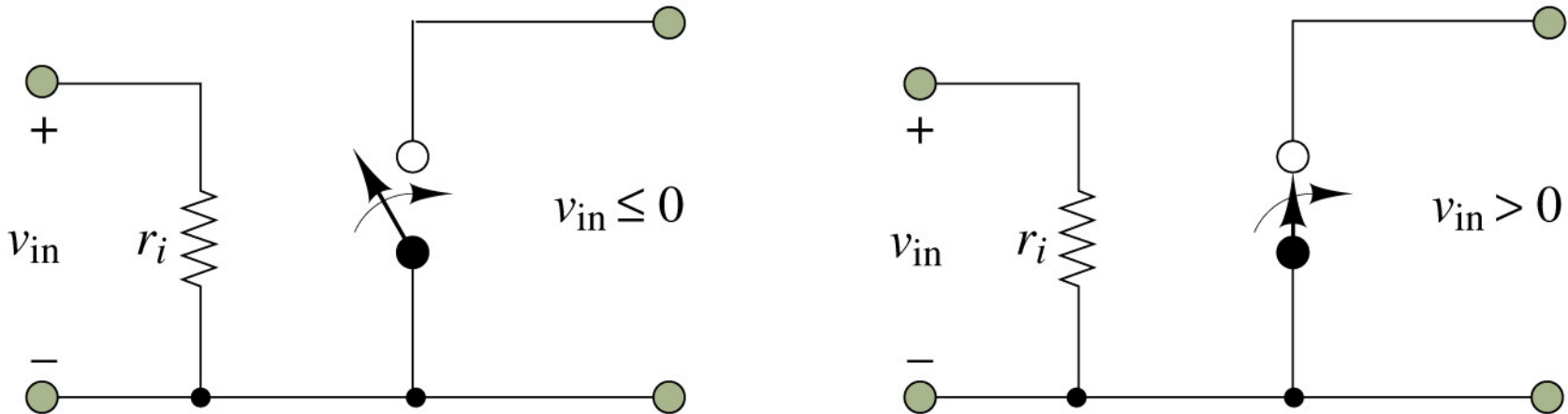


Voltage-controlled switch
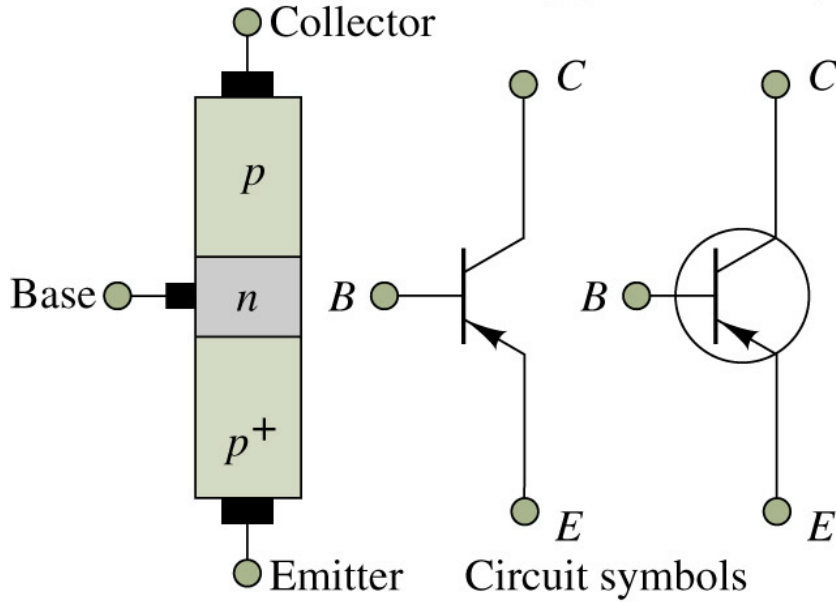
# Bipolar Junction Transistors

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




*pnp* transistor


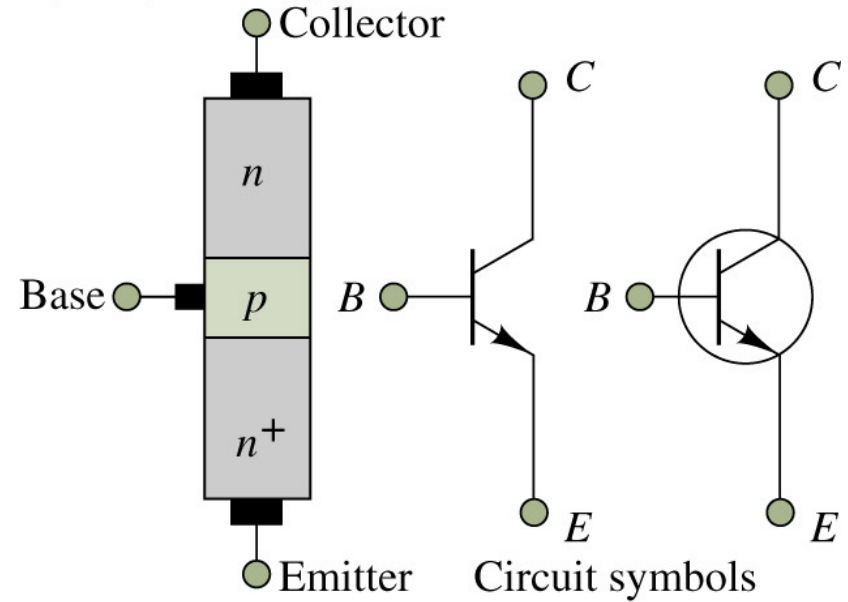


*npn* transistor
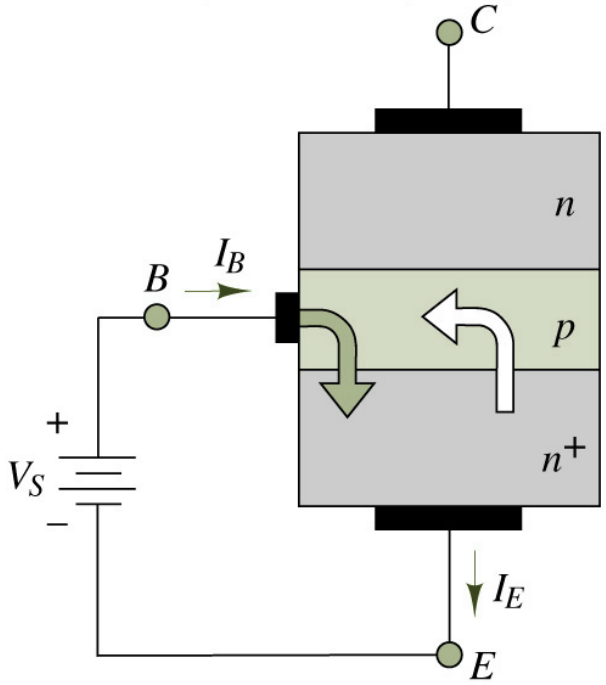
# Current Flow in an *npn* BJT

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




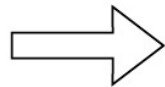
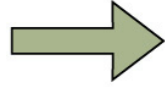
 = Electron flow  
 = Hole flow

The *BE* junction acts very much as an ordinary diode when the collector is open. In this case,  $I_B = I_E$ .
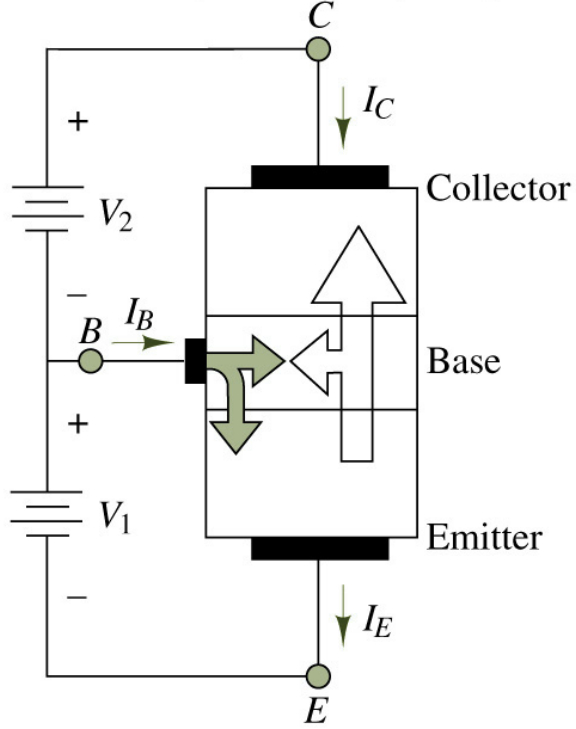
# Flow of Emitter Electrons into the Collector in an *npn* BJT

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



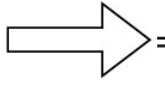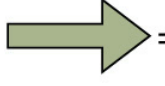
 = Electron flow  
 = Hole flow

When the *BC* junction is reverse-biased, the electrons from the emitter region are swept across the base into the collector.


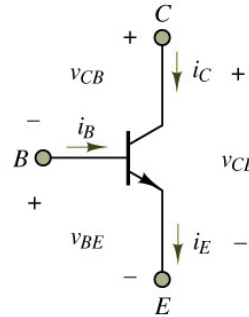
# Definition of BJT Voltages and Currents



Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.  
The operation of the BJT is defined  
in terms of two currents and two  
voltages:  $i_B$ ,  $i_C$ ,  $v_{CE}$ , and  $v_{BE}$ .



$$\text{KCL: } i_E = i_B + i_C$$
$$\text{KVL: } v_{CE} = v_{CB} + v_{BE}$$

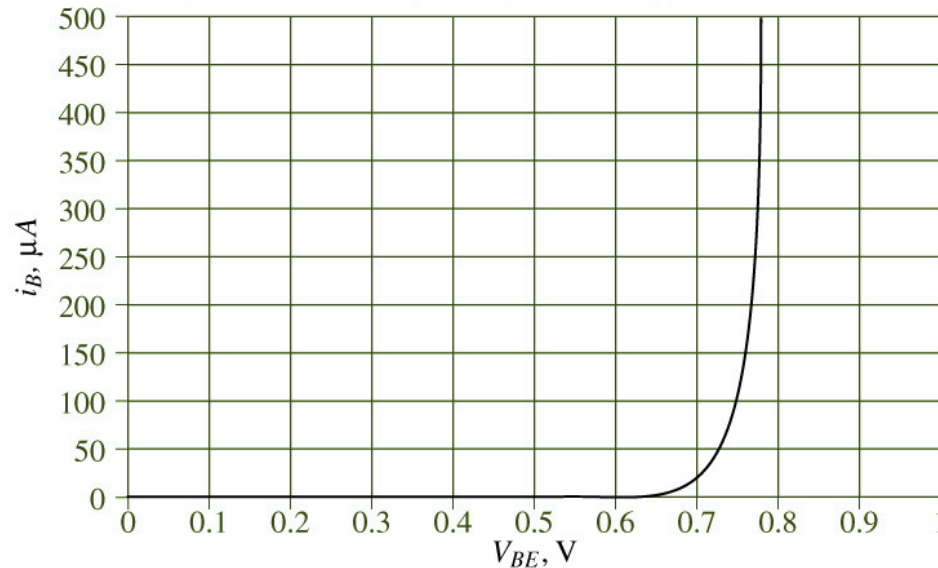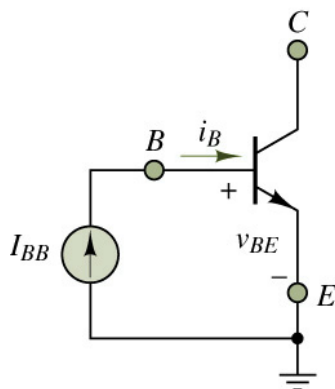
## The $BE$ Junction Open-Collector Curve

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


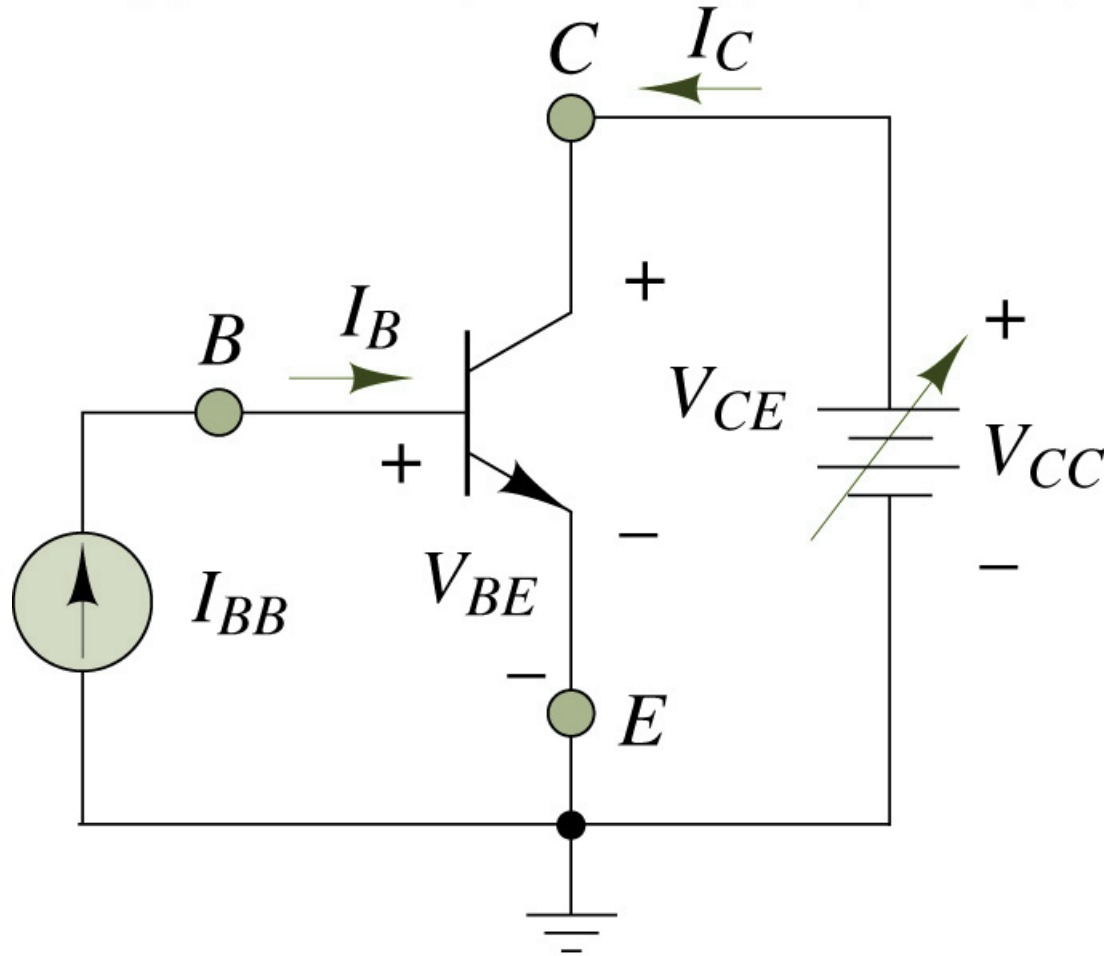
# Ideal Test Circuit to Determine the $i$ - $v$ Characteristic of a BJT


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



(a)

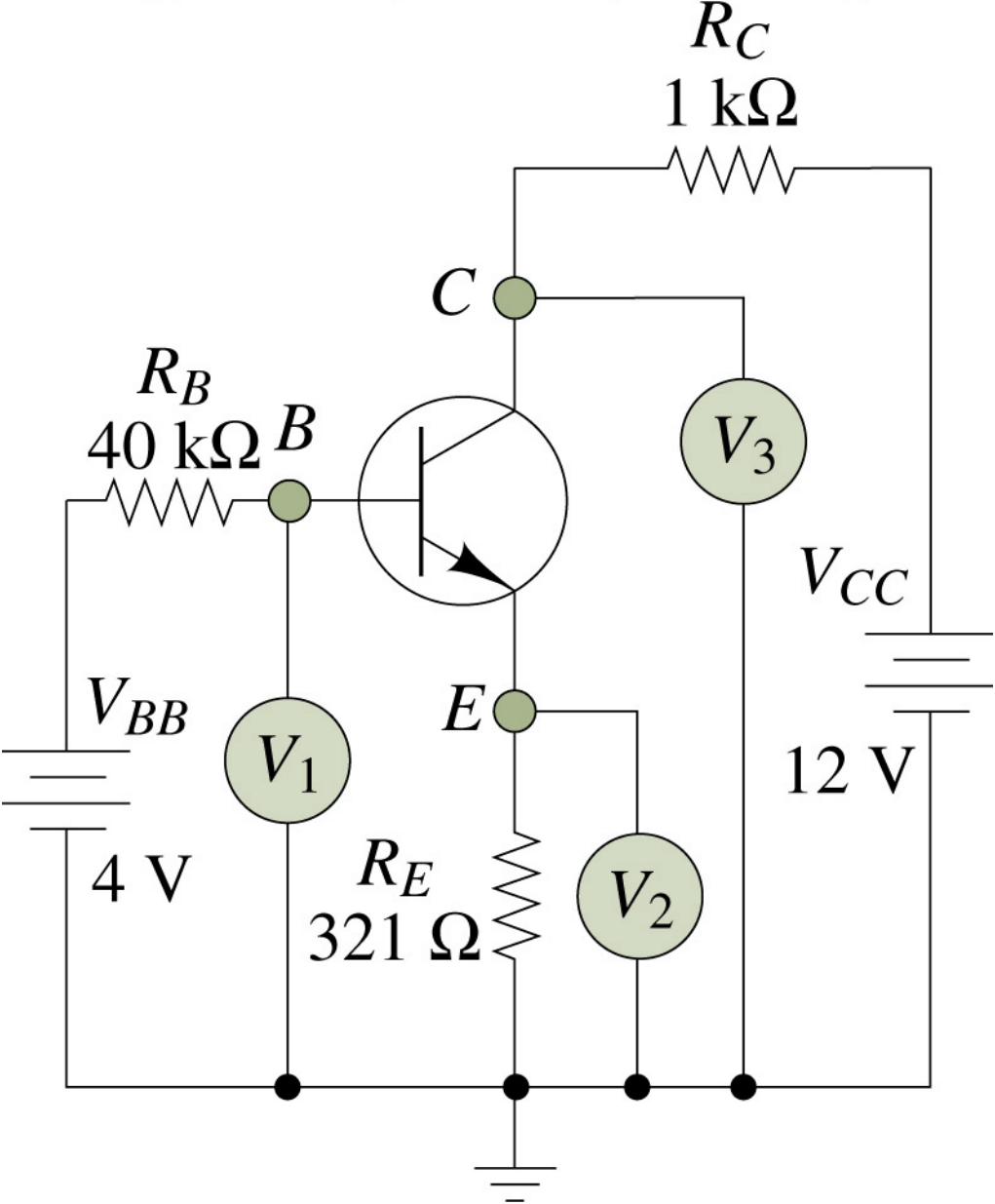
# Determination of the Operation Region of a BJT

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



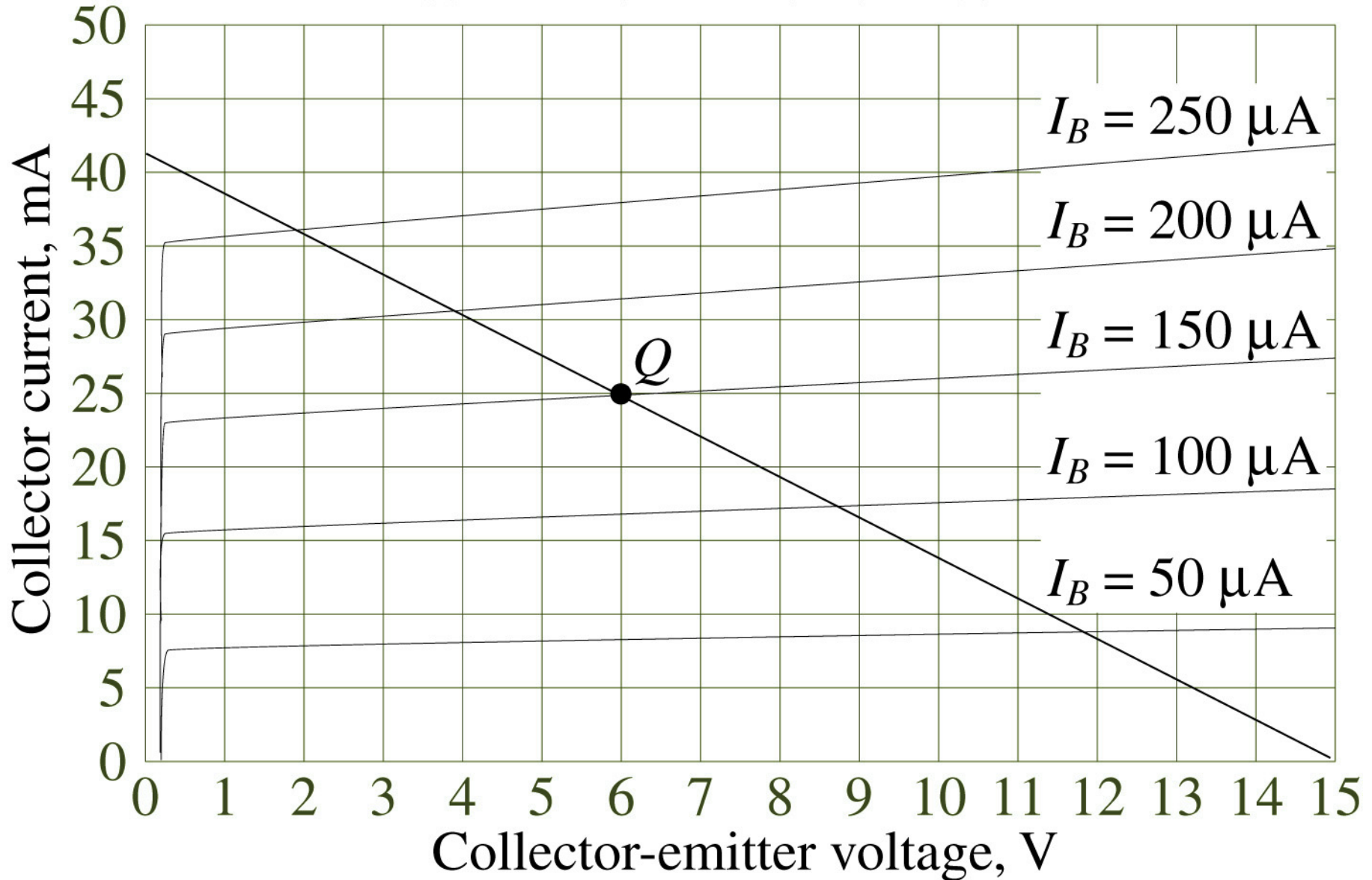
# Load-line Analysis of a Simplified BJT Amplifier

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



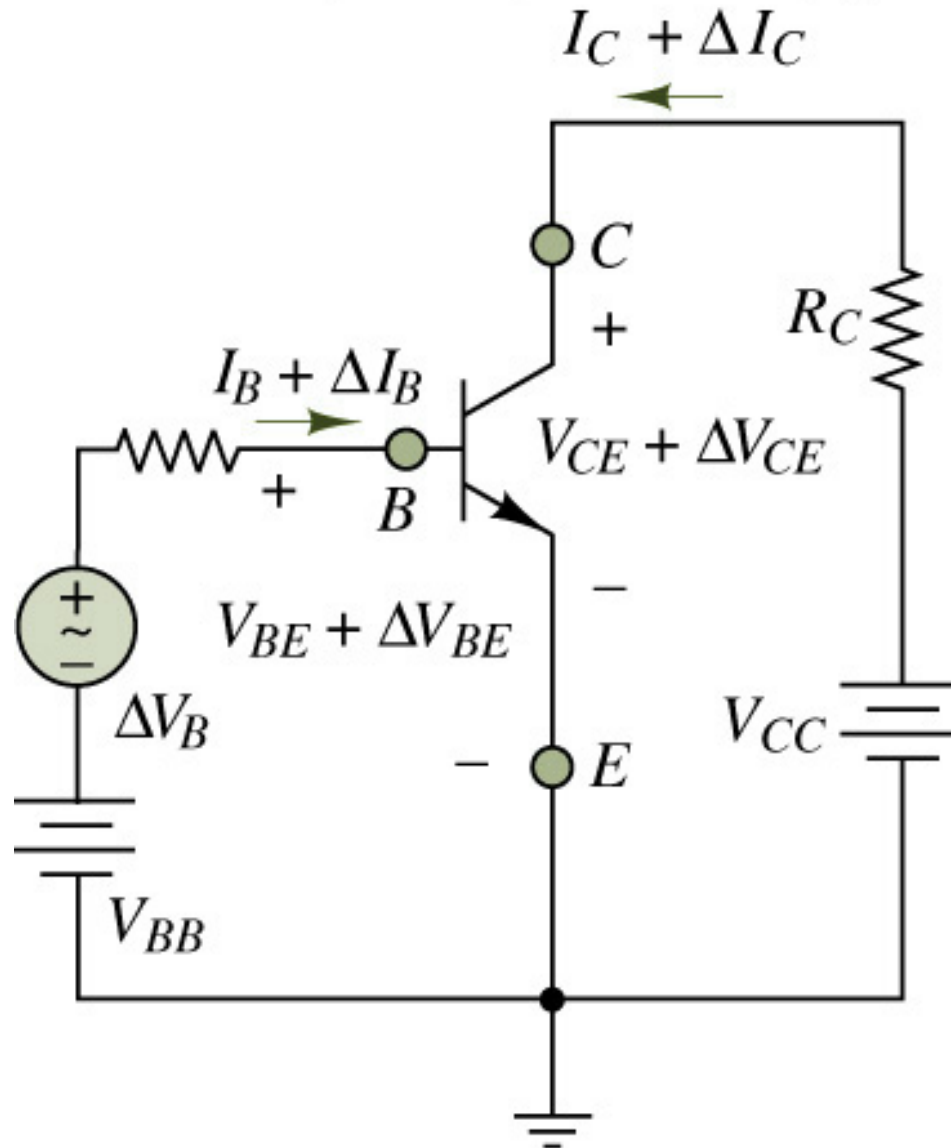
# Circuit Illustrating the Amplification Effect in a BJT

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.



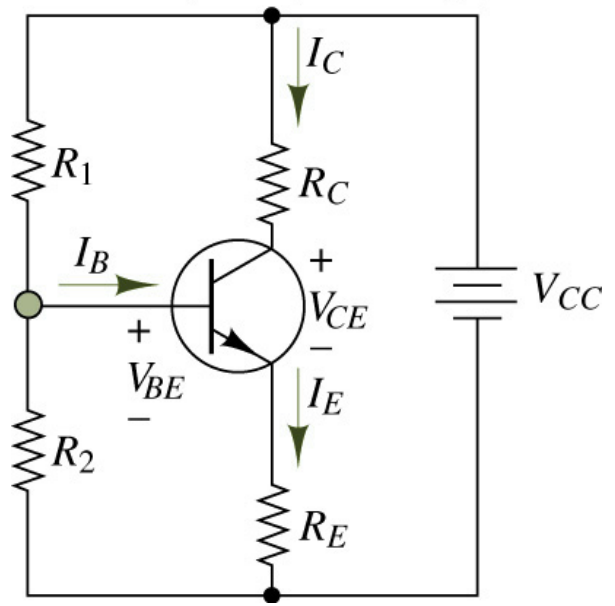
# Practical BJT Self-Bias DC Circuit

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



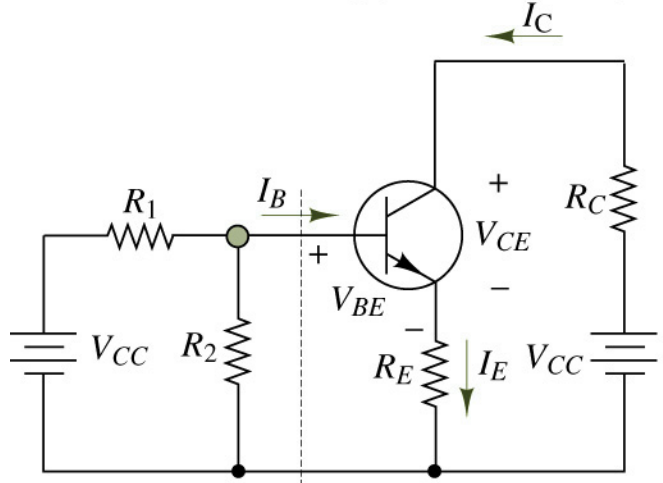
## DC Self-Bias Circuit Represented in Equivalent-Circuit Form

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



(a)

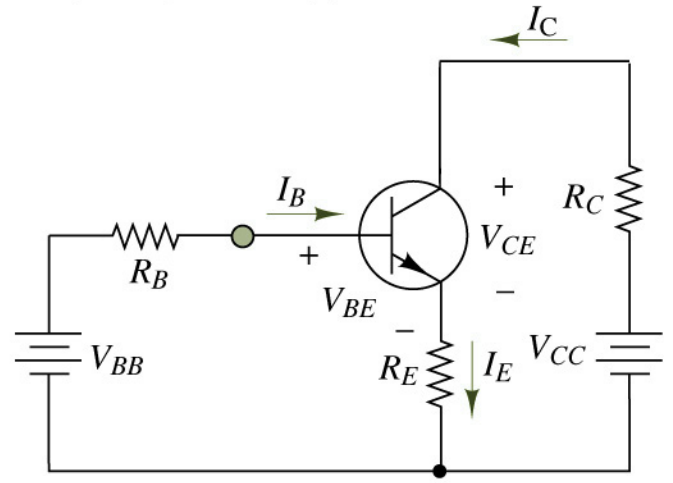

(b)

$$i_C = I_S e^{v_{BE}/V_T}$$

$$i_B = \frac{i_C}{\beta} = \left( \frac{I_S}{\beta} \right) e^{v_{BE}/V_T}$$

$$i_E = \frac{i_C}{\alpha} = \left( \frac{I_S}{\alpha} \right) e^{v_{BE}/V_T}$$

$$i_C = \alpha i_E; i_B = (1 - \alpha) i_E = \frac{i_E}{\beta + 1}$$

$$i_C = \beta i_B; i_E = (\beta + 1) i_B$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

- The basic principle involves the use of the voltage between two terminals to control the current flowing in the third terminal.
- Current is conducted by both electrons and holes, therefore the name bipolar.
- $\alpha$  is called the common-base current gain.
- $\beta$  is called the common-emitter current gain.

# DC Analysis of Transistor Circuits

## Common-Emitter Configuration



Electronic Circuit Analysis and Design, Neamem, 2001

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$


$$V_{CC} = I_C R_C + V_{CE}$$

$$V_{CE} = V_{CC} - I_C R_C$$

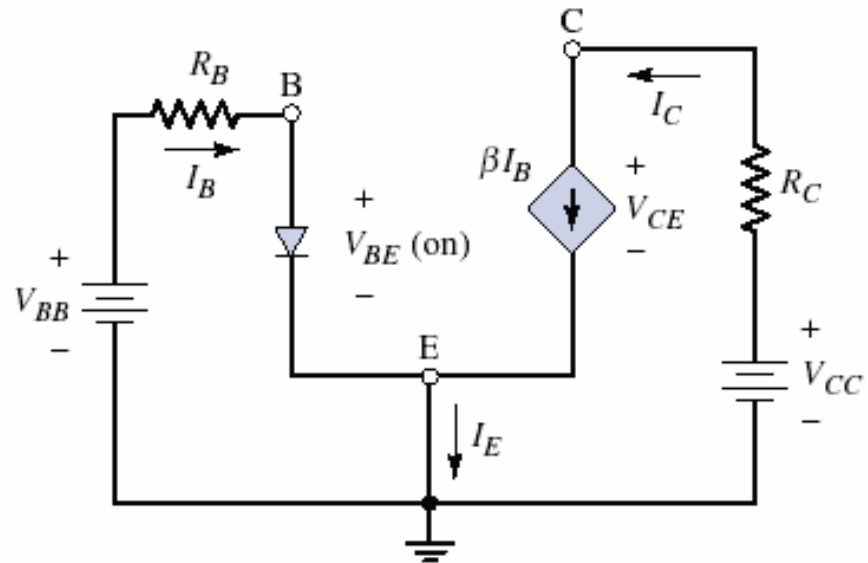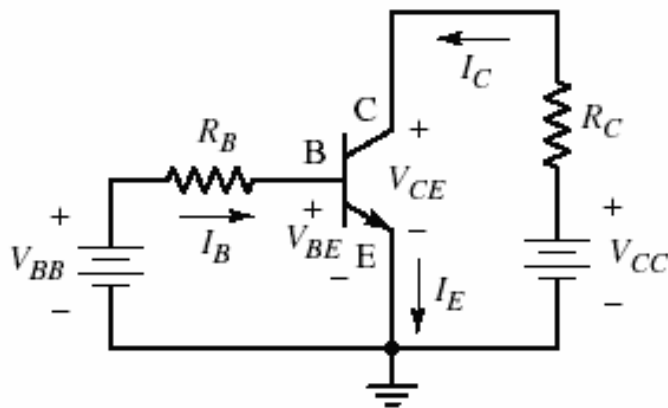



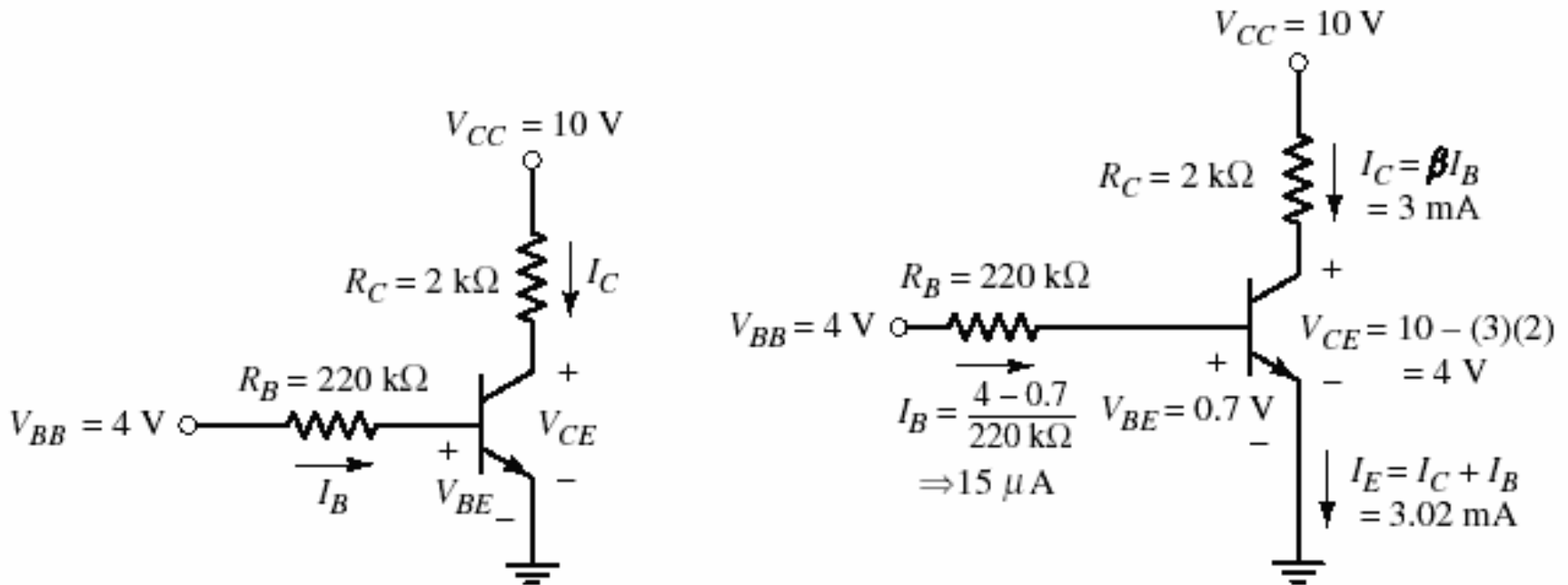**Example:** Calculate the base, collector, and emitter currents and the CE voltage for the following committer circuit when  $\beta = 200$ ,  $V_{BE} = 0.7$   
 (Electronic Circuit Analysis and Design, Neamem)



# Amplifier in a Circuits

## Block Diagram of a Compact Disc Player System

Neamen, Electronic Circuit Analysis and Design, McGraw Hill, 2001

