

## ELG4135: Tutorial on Chapter 12


Note, this is the dB in electronics.

### Q1 (12.5)


A low-pass filter is specified to have  $A_{\max} = 1$  dB and  $A_{\min} = 10$  dB. It is found that its specifications can be just met with a single-time-constant RC circuit having a time constant of 1 s and a dc transmission of unity. What must  $\omega_p$  and  $\omega_s$  of this filter be? What is the selectivity factor?

Solution:

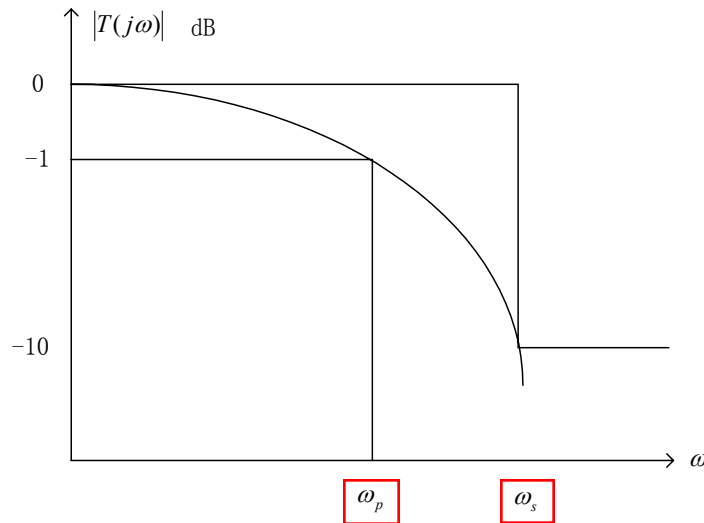The frequency response of the low-pass filter can be plotted as



An R-C low-pass filter can be plotted as

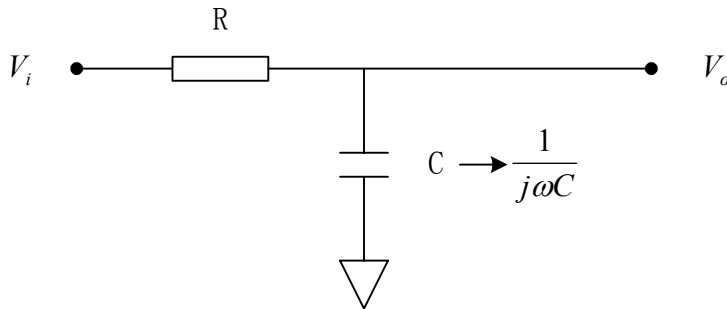

The voltage transfer function  $T(j\omega)$  is then

$$T(j\omega) = \frac{V_o}{V_i} = \frac{1}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$

Given  $\tau = RC = 1$  s,

$$T(j\omega) = \frac{1}{1 + j\omega}$$

The magnitude of  $T(j\omega)$  is then

$$|T(j\omega)| = \frac{1}{\sqrt{1 + \omega^2}}$$

At the pass-band edge:

$$|T(j\omega_p)| = 10^{\frac{-1}{20}}. \text{ (Note: } 10^{\frac{-1}{20}} \text{ is the linear scale of -1 dB loss.)}$$

$$\text{ie. } \frac{1}{\sqrt{1 + \omega_p^2}} = 10^{\frac{-1}{20}}$$

$$\Rightarrow \omega_p = 0.5088 \text{ rad/s}$$

At the stop-band edge:

$$|T(j\omega_s)| = 10^{\frac{-10}{20}}. \text{ (Note: } 10^{\frac{-10}{20}} \text{ is the linear scale of -10 dB loss.)}$$

$$\text{ie. } \frac{1}{\sqrt{1 + \omega_s^2}} = 10^{\frac{-10}{20}}$$

$$\Rightarrow \omega_s = 3 \text{ rad/s}$$


$$\Rightarrow \text{Selectivity} = \frac{\omega_s}{\omega_p} = 5.9$$

#

### Q2 (12.11)

Analyze the RLC network of Fig. P11.11 to determine its transfer function  $T(s) = \frac{V_o(s)}{V_i(s)}$  and hence its

poles and zeros.

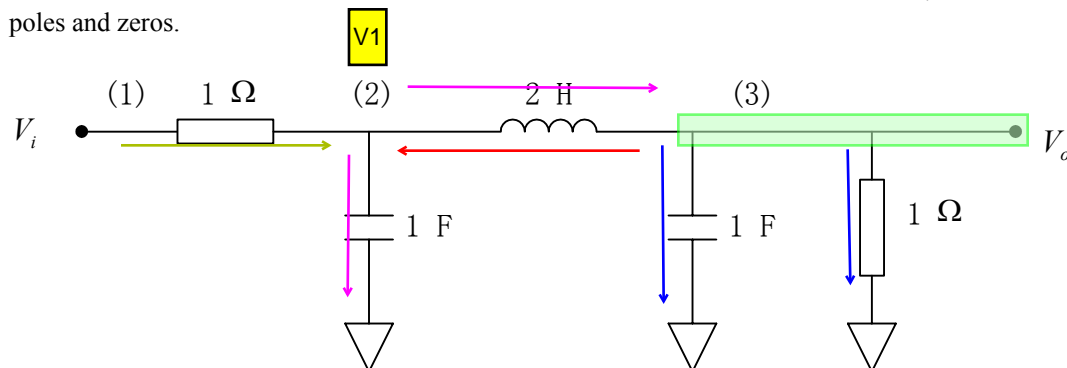

Solution:

The easiest way to solve the circuit is to use nodal analysis at nodes (1), (2) and (3).

At node (3),  $\Sigma I = 0$

$$\frac{V_o}{1} + \frac{V_o}{1/s} + \frac{V_o - V_1}{2s} = 0,$$

where  $V_1$  is the voltage at node (2).

$$\rightarrow V_1 = V_o(2s^2 + 2s + 1) \quad (a)$$

At node (2),  $\Sigma I = 0$

$$\frac{V_1 - V_i}{1} + \frac{V_1}{1/s} + \frac{V_1 - V_o}{2s} = 0,$$

$$\rightarrow V_1(2s^2 + 2s + 1) = V_o + 2sV_i \quad (b)$$

Substitute (a) to (b)

$$V_o(2s^2 + 2s + 1)^2 = V_o + 2sV_i$$

$$\Rightarrow T(s) = \frac{V_o(s)}{V_i(s)} = \frac{0.5}{s^3 + 2s^2 + 2s + 1}$$

$\Rightarrow$  There is no zero.

$\Rightarrow$  Poles are given by.

$$s^3 + 2s^2 + 2s + 1 = 0$$

$$(s + 1)(s^2 + s + 1) = 0$$

$$s = -1, s = -\frac{1}{2} \pm j\frac{\sqrt{3}}{2}$$

#

$$= - (V_i - V_1)/1$$

**Q3 (12.12)**

Determine the order  $N$  of the Butterworth filter for which  $A_{max} = 1$  dB,  $A_{min} \geq 20$  dB, and the selectivity ratio  $\frac{\omega_s}{\omega_p} = 1.3$ . What is the actual value of minimum stopband attenuation realized? If  $A_{min}$  is to be exactly 20 dB, to what value can  $A_{max}$  be reduced?

Solution:

From equation (12.15)

$$A(\omega_s) = 10 \log[1 + \varepsilon^2 (\frac{\omega_s}{\omega_p})^{2N}] = A_{min}$$

$$1 + \varepsilon^2 (\frac{\omega_s}{\omega_p})^{2N} = 10^{\frac{A_{min}}{10}}$$

$$(\frac{\omega_s}{\omega_p})^{2N} = \frac{10^{\frac{A_{min}}{10}} - 1}{\varepsilon^2}$$

$$\log[(\frac{\omega_s}{\omega_p})^{2N}] = \log[\frac{10^{\frac{A_{min}}{10}} - 1}{\varepsilon^2}]$$

$$N = \frac{\log[\frac{10^{\frac{A_{min}}{10}} - 1}{\varepsilon^2}]}{\log[(\frac{\omega_s}{\omega_p})^2]} \quad (a)$$

From equation (11.14), as  $A_{max} = 1$  dB,

$$\varepsilon = \sqrt{10^{\frac{A_{max}}{10}} - 1} = \sqrt{10^{\frac{1}{10}} - 1} = 0.5088$$

Substitute  $A_{min} \geq 20$  dB,  $\varepsilon$ , and the selectivity ratio  $\frac{\omega_s}{\omega_p} = 1.3$  into (a)

$$N \approx 11.3$$

=> Choose  $N=12$

The actual value of stopband attenuation can be calculated using  $N=12$  as

$$A(\omega_s) = 10 \log[1 + \varepsilon^2 (\frac{\omega_s}{\omega_p})^{2N}] = 27.35 \text{ dB}$$

If  $A_{min}$  is to be exactly 20 dB, from equation (12.15)

$$\varepsilon^2 = \frac{10^{\frac{A_{\min}}{10}} - 1}{\left(\frac{\omega_s}{\omega_p}\right)^{2N}} = 0.1824, \text{ with } A_{\min} = 20 \text{ dB and } N=12$$

From equation (11.13),

$$A_{\max} = 10 \log(1 + \varepsilon^2) = 0.73 \text{ dB}$$

#

#### Q4 (12.14)

Find the natural modes of a Butterworth filter with a 1-dB bandwidth of  $10^3$  rad/s and  $N=5$ .

Solution:

From equation (11.14), as  $A_{\max} = 1$  dB,

$$\varepsilon = \sqrt{10^{\frac{A_{\max}}{10}} - 1} = \sqrt{10^{\frac{1}{10}} - 1} = 0.5088$$


And  $\omega_p = 10^3$  rad/s,  $N=5$ , the solutions can be found graphically. (The method is shown in Fig. 11.10)

The radius of the circle is  $\omega_0 = \omega_p \left(\frac{1}{\varepsilon}\right)^{1/N} = 873.59$

$$P_1 = \omega_0 e^{\pm j\left(\frac{\pi}{2} + \frac{\pi}{2N}\right)} = -269.96 \pm j830.84$$

$$P_2 = \omega_0 e^{\pm j\left(\frac{\pi}{2} + \frac{\pi}{2N} + \frac{\pi}{N}\right)} = -706.75 \pm j513.49$$

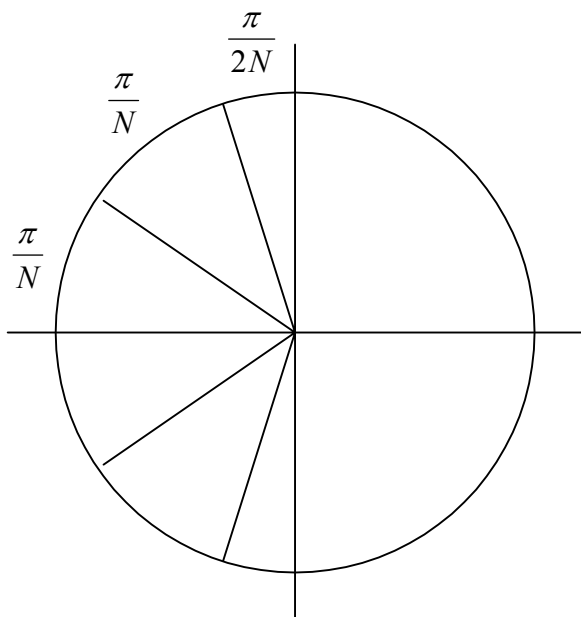
$$P_3 = \omega_0 e^{\pm j(\pi)} = -873.59$$



**Q5 (12.22)**

By cascading a first-order op amp-RC low-pass circuit with a first-order op amp-RC high-pass circuit one can design a wideband bandpass filter. Provide such a design for the case the midband gain is **12 dB** and the 3-dB bandwidth extends from 100 Hz to 10 kHz. Select appropriate component values under the constraint **that no resistors higher than 100 kohms** are to be used, and the input resistance is to be as high as possible.

Solution:

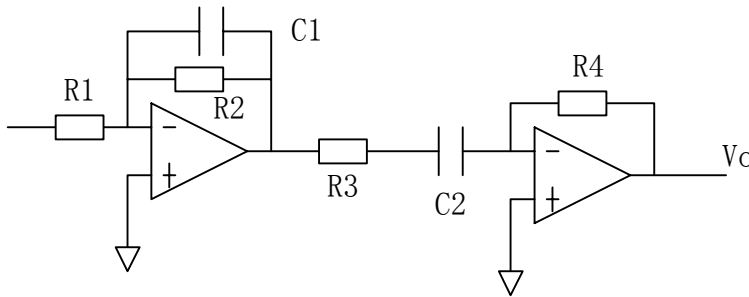

**Gain** =  $10^{12/20} = 3.98 \approx 4$

Want  $R_i = R_1$  large, so  **$R_1 = 100 \text{ k}\Omega$**

Total gain =  $A_{lp} \cdot A_{hp} = 4$

$A_{lp} = -R_2/R_1 \Rightarrow R_2 = -A_{lp} \cdot R_1$  and  **$R_2 < 100 \text{ k}\Omega$** , so

when  $R_1$  and  $R_2$  are both selected as 100 k, then  $A_{lp} = -R_2/R_1 = -1$ .

$A_{lp} = -1$ ,  $R_2 = 100 \text{ k}\Omega$

From Fig. 11.14,  $R_2 C_1 = \frac{1}{\omega_{0,lp}}$ ,

$C_1 = \frac{1}{R_2 \omega_{0,lp}} = \frac{1}{2\pi(10 \times 10^3)100 \times 10^3} = 0.159 \text{ nF}$

C1 min.

"the 3-dB bandwidth extends from 100 Hz to 10 kHz."

$A_{hp} = -4$ ,  **$R_4 = 100 \text{ k}\Omega$** ,  **$R_3 = 25 \text{ k}\Omega$**

From Fig. 11.14,  $R_3 C_2 = \frac{1}{\omega_{0,hp}}$ ,

$C_2 = \frac{1}{R_3 \omega_{0,hp}} = \frac{1}{2\pi \times (100) \times 25 \times 10^3} = 63.7 \text{ nF}$

C2 max.

Handwritten red annotations: a question mark and the number 3.