


**ELG3331: Design Problems for Instrumentations**  
**Assignment Based on DAC, ADC and Comparators**  
**Sections 15.4 and 15.5 of the textbook**

**Problem 1**

Design an alarm system that is to be set off when room temperature exceeds  $50^{\circ}\text{C}$ . Given to you are a temperature-to-voltage- transducer for which  $50^{\circ}\text{C}$  produces a voltage  $v_1 = 5$  V. The alarm sounds when -15 V is applied, and it is silent when +15 V is applied.

**Solution**

We should provide a circuit that monitors the transducer voltage and apply the proper voltage to the alarm. We need a circuit that compares  $v_1$  with a 5-V reference and changes its output suddenly when  $v_1$  exceeds 5 V. Such a circuit is called a **comparator**. When  $v_1$  exceeds 5 V,  $v_o$  falls from 15 to -15.

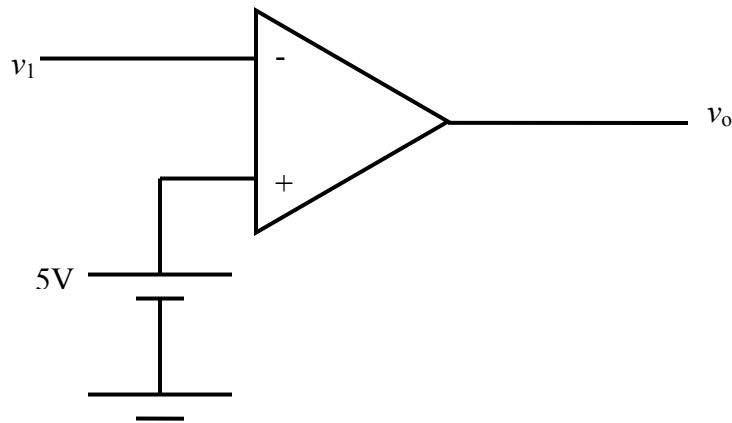


**Problem 2**

Design a digital-to-analog (DAC) that produces an analog output voltage  $v_o$  equal -1 V times the 4-bit number at the input.

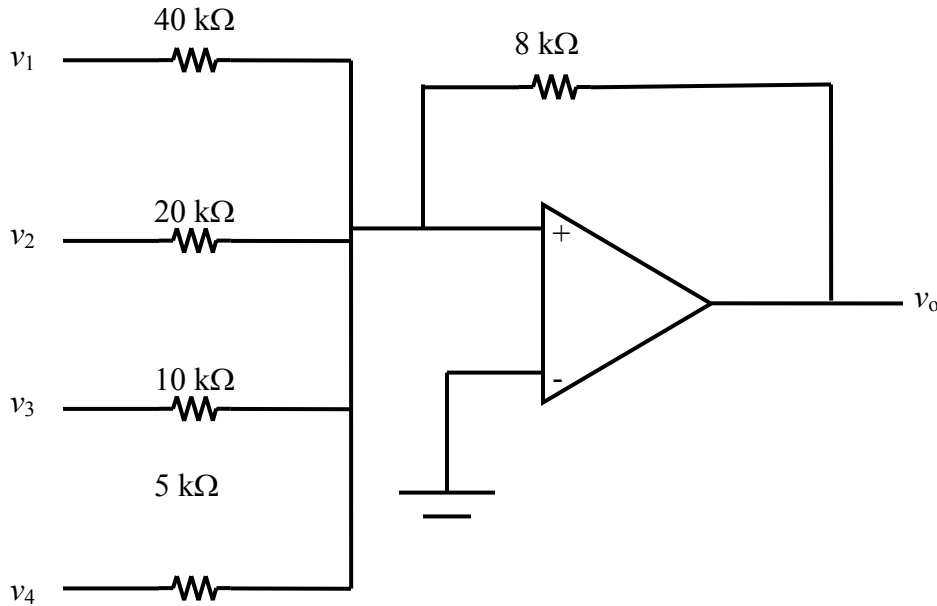**Solution**

The bits (least significant to most significant) are represented by  $v_1, v_2, v_3,$  and  $v_4$ . Logic 1 is represented by 5 V and logic 0 by 0 V. One possible design is shown in the following Figure.



$v_4$	$v_3$	$v_2$	$v_1$	$v_o$
0	0	0	0	0
0	0	0	5	-1
0	0	5	0	-2
0	0	5	5	-3
0	5	0	0	-4
0	5	0	5	-5
0	5	5	0	-6
0	5	5	5	-7
5	0	0	0	-8
5	0	0	5	-9
5	0	5	0	10
5	0	5	5	-11
5	5	0	0	-12
5	5	0	5	-13
5	5	5	0	-14
5	5	5	5	-15

In summation, each input receives a different gain or weighting

$v_o = -1.6v_4 - 0.8v_3 - 0.4v_2 - 0.2v_1$
--

**Problem 3**

Draw the circuit diagram for a 4-bit DAC and determine the expression relating  $v_o$  to the binary input bits.

**Problem 4**

Consider the DAC given in Problem 3. What value of  $R_F$  will give the output range  $-10\text{ V} \leq v_o \leq 0\text{ V}$

**Problem 5**

Consider the DAC given in Problem 3. What value of  $R_F$  will give the output range  $-15\text{ V} \leq v_o \leq 0\text{ V}$

**Problem 6**

Using a DAC model. Design a 4-bit DAC whose output is given by

$$v_o = \frac{1}{10}(8b_3 + 4b_2 + 2b_1 + b_0)\text{ V}$$

**Problem 7**

A data acquisition uses a DAC with a range of  $\pm 10\text{ V}$ . and a resolution of  $0.04\text{ V}$ . How many bits must be present in the DAC?

**Problem 8**

How many comparators are needed in a 4-bit flash ADC?

**Problem 9**

Consider the ADC (AD574) with the following specifications:  $V_{CC} = 15\text{ V}$ ;  $0 \leq V_{in} \leq 15\text{ V}$ . What is the accuracy (in volts) of the AD574? What is the highest signal that can be converted by this ADC without violating Nyquist criterion if the conversion time is  $35\text{ }\mu\text{s}$ ?

**Problem 10**

Sketch the input and output waveforms of a comparator with  $V_{ref} = 0.8\text{ V}$ .

**Problem 11**

Solve problem 15.71 in the textbook.